



"ज्ञान, विज्ञान आणि सुसंस्कार यासाठी शिक्षण प्रसार"

शिक्षण महर्षी-डॉ. साळुंखेबापूजी

**Shri Swami Vivekanand Shikshan Sanstha's
Dattajirao Kadam Arts, Science & Commerce
College, Ichalkaranji**



DEPARTMENT OF PHYSICS

QUESTION BANK

B. Sc. – III, PHYSICS (Paper-XII), DSE-E4 Digital and Analog Circuits and Instrumentation

Multiple choice questions.

1. Which of the following is a universal gate?

- a) AND
- b) OR
- c) NAND
- d) XOR

Answer: c) NAND

2. Which logic gate provides an output of 1 only when the inputs are different?

- a) AND
- b) NOR
- c) XOR
- d) NAND

Answer: c) XOR

3. What is the Boolean expression for a NOR gate?

- a) $A + B$
- b) $(A + B)'$
- c) $A \cdot B$
- d) $(A \cdot B)'$

Answer: b) $(A + B)'$

4. Which of the following represents De Morgan's theorem?

a) $(A + B)' = A' + B'$

b) $(A \cdot B)' = A' + B'$

c) $(A + B)' = A' \cdot B'$

d) $A' + B' = A \cdot B$

Answer: c) $(A + B)' = A' \cdot B'$

5. What is the function of a flip-flop?

a) Amplification

b) Counting

c) Storage

d) Both b and c

Answer: d) Both b and c

6. Which flip-flop is known as a "universal flip-flop"?

a) R-S

b) D

c) J-K

d) T

Answer: c) J-K

7. Which flip-flop has an undefined state when both inputs are 1?

a) R-S

b) J-K

c) D

d) T

Answer: a) R-S

8. How many inputs does a full adder have?

a) 2

b) 3

c) 4

d) 5

Answer: b) 3

9. The sum output of a half adder is given by which logic function?

- a) AND
- b) OR
- c) XOR
- d) NAND

Answer: c) XOR

10. A 4-bit parallel adder consists of how many full adders?

- a) 1
- b) 2
- c) 3
- d) 4

Answer: d) 4

11. In a CE amplifier, the output is

- a) In phase with the input
- b) 180° out of phase with the input
- c) Always zero
- d) Doubled in magnitude

Answer: b) 180° out of phase with the input

12. The AC load line represents

- a) DC operating point
- b) Variation in voltage and current with signal
- c) Amplifier efficiency
- d) Amplifier gain

Answer: b) Variation in voltage and current with signal

13. What is the significance of the Q point in an amplifier?

- a) Determines the stability of the amplifier
- b) Reduces distortion
- c) Sets the biasing conditions
- d) All of the above

Answer: d) All of the above

14. Which feedback provides sustained oscillations in an oscillator?

- a) Negative feedback
- b) Positive feedback
- c) No feedback
- d) Both positive and negative feedback

Answer: b) Positive feedback

15. What is the main requirement for an oscillator to start oscillating?

- a) Barkhausen criterion
- b) High gain
- c) Low distortion
- d) High efficiency

Answer: a) Barkhausen criterion

16. Which oscillator uses an inductor-capacitor (LC) tank circuit?

- a) Phase shift
- b) Wien bridge
- c) Colpitts
- d) Schmitt trigger

Answer: c) Colpitts

17. Which oscillator is most stable in frequency?

- a) Colpitts
- b) Hartley
- c) Phase shift
- d) Crystal

Answer: d) Crystal

18. Which oscillator uses a tapped inductor?

- a) Colpitts
- b) Hartley
- c) Phase shift
- d) Crystal

Answer: b) Hartley

19. Which part of a CRO generates an electron beam?

- a) Deflection plates
- b) Cathode
- c) Grid
- d) Anode

Answer: b) Cathode

20. The primary function of a CRO is to display

- a) Sound waves
- b) Voltage signals
- c) Mechanical motion
- d) Temperature variations

Answer: b) Voltage signals

21. Lissajous figures on a CRO screen are used to measure

- a) Resistance
- b) Frequency and phase difference
- c) Voltage
- d) Current

Answer: b) Frequency and phase difference

22. An operational amplifier has

- a) One input, one output
- b) Two inputs, one output
- c) One input, two outputs
- d) Two inputs, two outputs

Answer: b) Two inputs, one output

23. The input impedance of an ideal Op-Amp is

- a) 0
- b) Low
- c) High
- d) Infinite

Answer: d) Infinite

24. What is the voltage gain of a unity gain buffer amplifier?

- a) 0
- b) 1
- c) 10
- d) 100

Answer: b) 1

25. Which Op-Amp circuit performs mathematical differentiation?

- a) Differentiator
- b) Integrator
- c) Adder
- d) Subtractor

Answer: a) Differentiator

26. Which pin of IC 555 is the trigger input?

- a) Pin 1
- b) Pin 2
- c) Pin 3
- d) Pin 4

Answer: b) Pin 2

27. What is the duty cycle of a 555 timer in astable mode?

- a) 25%
- b) 50%
- c) 75%
- d) Variable

Answer: d) Variable

28. A monostable multivibrator using a 555 timer has

- a) One stable state
- b) Two stable states
- c) No stable state
- d) Multiple stable states

Answer: a) One stable state

29. A NOR gate can be used to create which of the following?

- a) AND gate
- b) OR gate
- c) NOT gate
- d) All of the above

Answer: d) All of the above

30. What is the output of a NAND gate when both inputs are HIGH?

- a) HIGH
- b) LOW
- c) Undefined
- d) Cannot be determined

Answer: b) LOW

31. The XOR gate is also known as

- a) Difference gate
- b) Parity gate
- c) Equality gate
- d) Inversion gate

Answer: b) Parity gate

32. The main disadvantage of an R-S flip-flop is

- a) It is slow
- b) It has a race condition
- c) It requires many components
- d) It is expensive

Answer: b) It has a race condition

33. Which circuit converts binary addition directly to decimal output?

- a) Half adder
- b) Full adder
- c) BCD adder
- d) XOR adder

Answer: c) BCD adder

34. Which component stabilizes the Q-point in a transistor amplifier?

- a) Resistor
- b) Capacitor
- c) Inductor
- d) Transformer

Answer: a) Resistor

35. The voltage gain of a transistor amplifier is given by

- a) Collector resistance/Base resistance
- b) Collector resistance/Emitter resistance
- c) Base resistance/Collector resistance
- d) Emitter resistance/Base resistance

Answer: b) Collector resistance/Emitter resistance

36. Which of the following amplifiers has the highest voltage gain?

- a) Common Base
- b) Common Collector
- c) Common Emitter
- d) Emitter Follower

Answer: c) Common Emitter

37. In a transistor amplifier, which load line determines the output signal swing?

- a) DC load line
- b) AC load line
- c) Both a and b
- d) None of the above

Answer: b) AC load line

38. A transistor amplifier introduces a phase shift of

- a) 0°
- b) 90°
- c) 180°
- d) 270°

Answer: c) 180°

39. Which type of oscillator is commonly used in RF applications?

- a) Wien Bridge
- b) Phase Shift
- c) Crystal
- d) Colpitts

Answer: c) Crystal

40. Which oscillator circuit uses a capacitor divider network for feedback?

- a) Hartley
- b) Colpitts
- c) Phase shift
- d) Wien bridge

Answer: b) Colpitts

41. What is the main function of a tank circuit in an oscillator?

- a) Amplification
- b) Signal modulation
- c) Energy storage and oscillation
- d) Waveform shaping

Answer: c) Energy storage and oscillation

42. Which feedback condition is required for an oscillator?

- a) Negative feedback with gain < 1
- b) Positive feedback with gain = 1
- c) Negative feedback with gain > 1
- d) Positive feedback with gain > 1

Answer: b) Positive feedback with gain = 1

43. Which of the following is NOT a part of a CRT?

- a) Electron gun
- b) Deflection system
- c) Time base generator
- d) Diode bridge

Answer: d) Diode bridge

44. Which electrode in a CRT controls the brightness of the display?

- a) Cathode
- b) Control grid
- c) Deflection plates
- d) Anode

Answer: b) Control grid

45. The deflection sensitivity of a CRO depends on

- a) Plate voltage
- b) Screen size
- c) Deflection plate spacing
- d) All of the above

Answer: d) All of the above

46. Lissajous figures help in determining

- a) Voltage
- b) Phase difference
- c) Resistance
- d) Power

Answer: b) Phase difference

47. In a differential amplifier, the output depends on

- a) Sum of input voltages
- b) Difference of input voltages
- c) Product of input voltages
- d) None of the above

Answer: b) Difference of input voltages

48. The gain of an inverting Op-Amp is given by

- a) $-R_f/R_{in}$
- b) R_{in}/R_f
- c) $1 + (R_f/R_{in})$
- d) $1 - (R_f/R_{in})$

Answer: a) $-R_f/R_{in}$

49. In a 555 timer, the capacitor connected to pin 5 is used for

- a) Resetting the timer
- b) Controlling voltage levels
- c) Increasing frequency
- d) Decreasing frequency

Answer: b) Controlling voltage levels

50. A 555 timer in astable mode generates

- a) A single pulse
- b) A continuous square wave
- c) A triangular wave
- d) A sine wave

Answer: b) A continuous square wave