

# DeMorgan's Theory

- **DeMorgan's Theorem** is mainly used to solve the various Boolean algebra expressions.
- The Demorgan's theorem defines the uniformity between the gate with the same inverted input and output.
- It is used for implementing the basic gate operation likes NAND gate and NOR gate.
- The Demorgan's theorem mostly used in digital programming and for making digital circuit diagrams.
- There are two DeMorgan's Theorems.

# DeMorgan's first Theory

- DeMorgan's first theory states that a NOR gate and a bubbled AND gate are equivalent. Both truth tables are identical, which means that two circuits are logically equivalent.


- the equation:

$$\overline{A + B} = \overline{A} \cdot \overline{B}$$

NOR = Bubbled AND

- The LHS of this theorem represents a NOR gate with inputs A and B, whereas the RHS represents an AND gate with inverted inputs.
- This AND gate is called a Bubbled AND.

# DeMorgan's first Theory

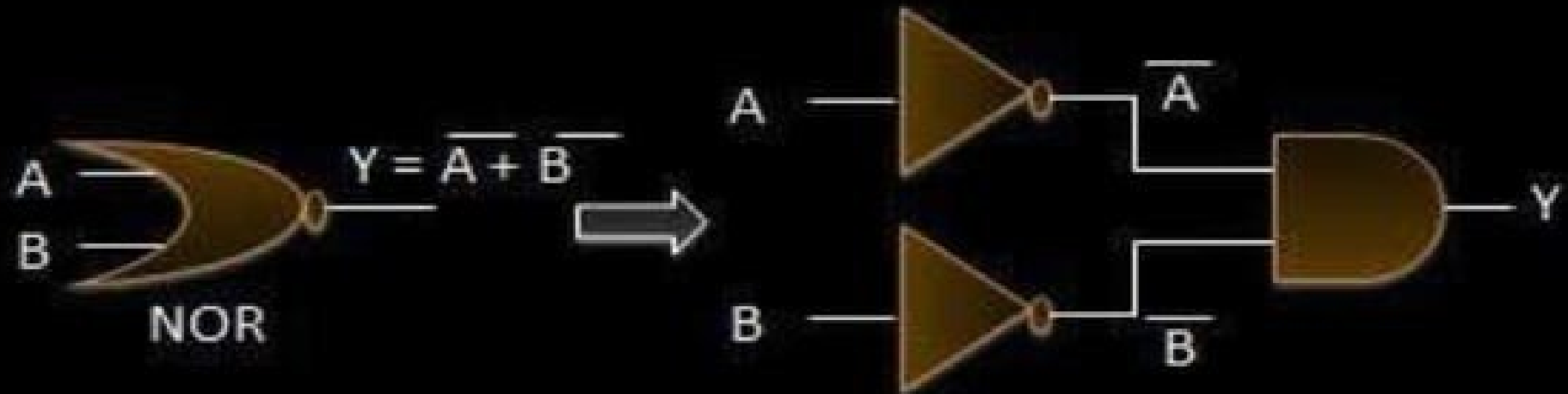

NOR  $\equiv$  Bubbled AND



Bubbled AND

# DeMorgan's first Theory

- Table showing verification of the De Morgan's first theorem –

A	B	$\overline{A+B}$	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	1	1	1	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	0


# DeMorgan's Second Theory

- DeMorgan's Second Theorem states that the NAND gate is equivalent to a bubbled OR gate.
- The Boolean expression for the NAND gate is given by the equation shown below:

$$\overline{A \cdot B} = \overline{A} + \overline{B}$$

- The left hand side (LHS) of this theorem represents a **NAND** gate with inputs A and B, whereas the right hand side (RHS) of the theorem represents an **OR** gate with inverted inputs.
- This OR gate is called as **Bubbled OR**.

# DeMorgan's Second Theory

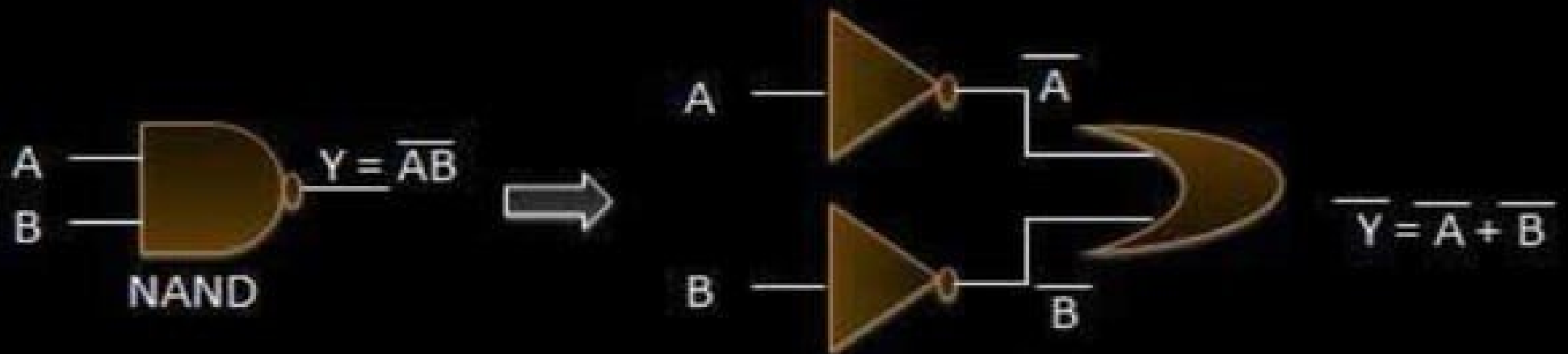

NAND  $\equiv$  Bubbled OR



Bubbled OR

# DeMorgan's second Theory

- Table showing verification of the De Morgan's second theorem –

A	B	$\overline{AB}$	$\overline{A}$	$\overline{B}$	$\overline{A} + \overline{B}$
0	0	1	1	1	1
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	0	0	0