

So each R-C stage will provide 60° phase shift.


Expression for R-C phase shift:-

$$f_0 = \frac{1}{2\pi RC \sqrt{6 + 4\frac{R_c}{R}}}$$

when we can not use transistor then  $R_c = 0$

$$f_0 = \frac{1}{2\pi RC \sqrt{6}}$$

\* Wein's Bridge Oscillator:-

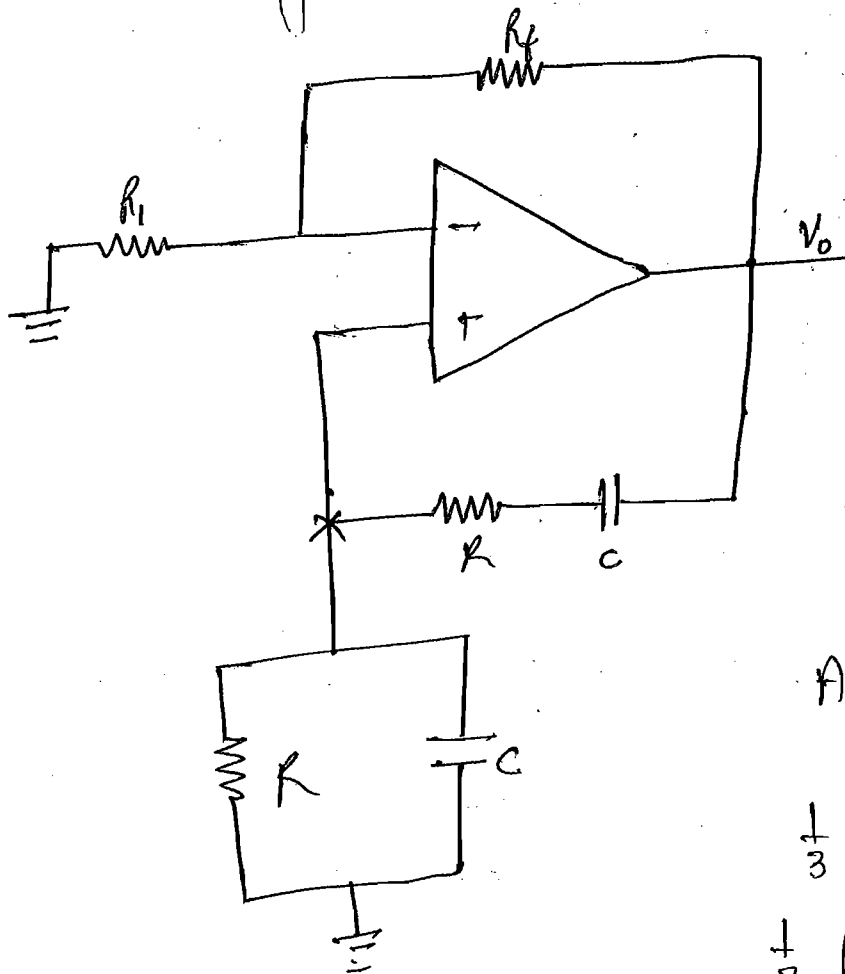

$$A = 1 + \frac{R_f}{R_i}$$

$$\frac{1}{3} A \geq 1$$


$$\frac{1}{3} \left( 1 + \frac{R_f}{R_i} \right) \geq 1$$

$$\omega = \frac{1}{RC} \quad , \quad f = \frac{1}{2\pi RC}$$

$$Q_0 \quad \boxed{f_0 = \frac{1}{2\pi RC}}$$

B.A.  
Q. 59

Q. 59

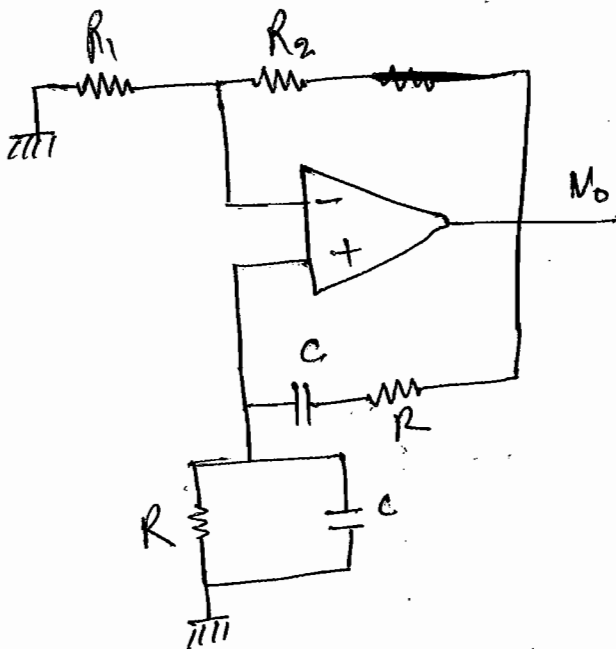

$$C = 0.01 \mu\text{F}$$

$$R_1 = 1 \text{ k}\Omega$$

$$f_0 = 300 \text{ Hz}$$

$$\therefore f_0 = \frac{1}{2\pi RC}$$

$$R = \frac{1}{2\pi f_0 C} = \frac{1}{2\pi \times 300 \times 0.01 \mu\text{F}}$$

$$= \frac{10^8}{300 \times 2\pi} = \frac{10^6}{6\pi}$$

$$= \underline{\underline{53 \text{ k}\Omega}} \quad 53 \times 10^3 \Omega$$

$$\boxed{R = 53 \text{ k}\Omega}$$

$$\frac{1}{3} A \geq 1$$

$$\frac{1}{3} \left( 1 + \frac{R_2}{R_1} \right) = 1 \quad (\text{Worst Case})$$


$$1 + \frac{R_2}{R_1} = 3$$

$$\frac{R_2}{R_1} = 2$$

$$\frac{R_2}{12} = 2$$

$$\boxed{R_2 = 24} \quad \underline{\underline{\text{Ans}}}$$

\* Hartley Oscillator :-

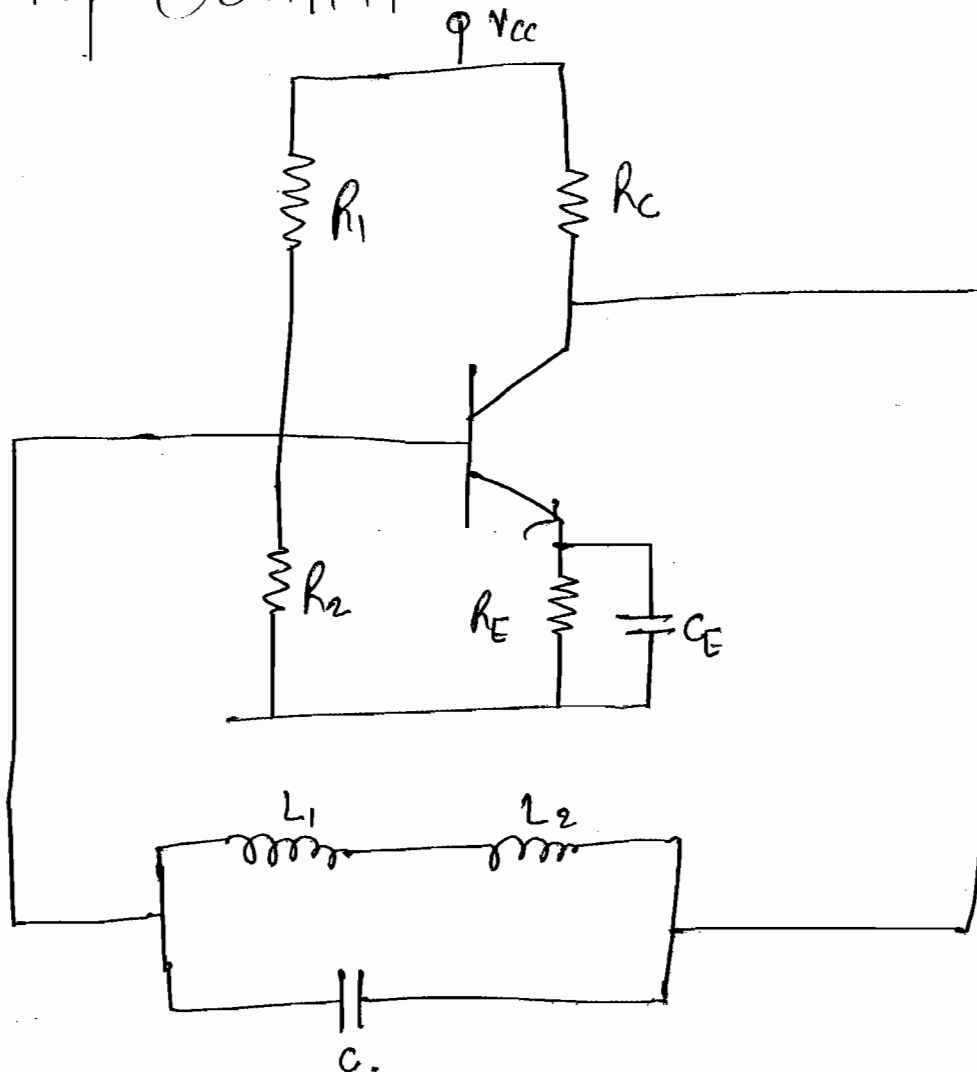

The output of G.E. Configuration provides a phase shift of  $180^\circ$  additional phase shift in tank circuit is used so that it can provide a phase shift of  $180^\circ$ . To provide sustained oscillation.

$$X_L = X_C$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$


$$\omega = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{L_{eq} C_{eq}}}$$

$$f_0 = \frac{1}{2\pi\sqrt{(L_1 + L_2)C}}$$

# Collpits Oscillator :-

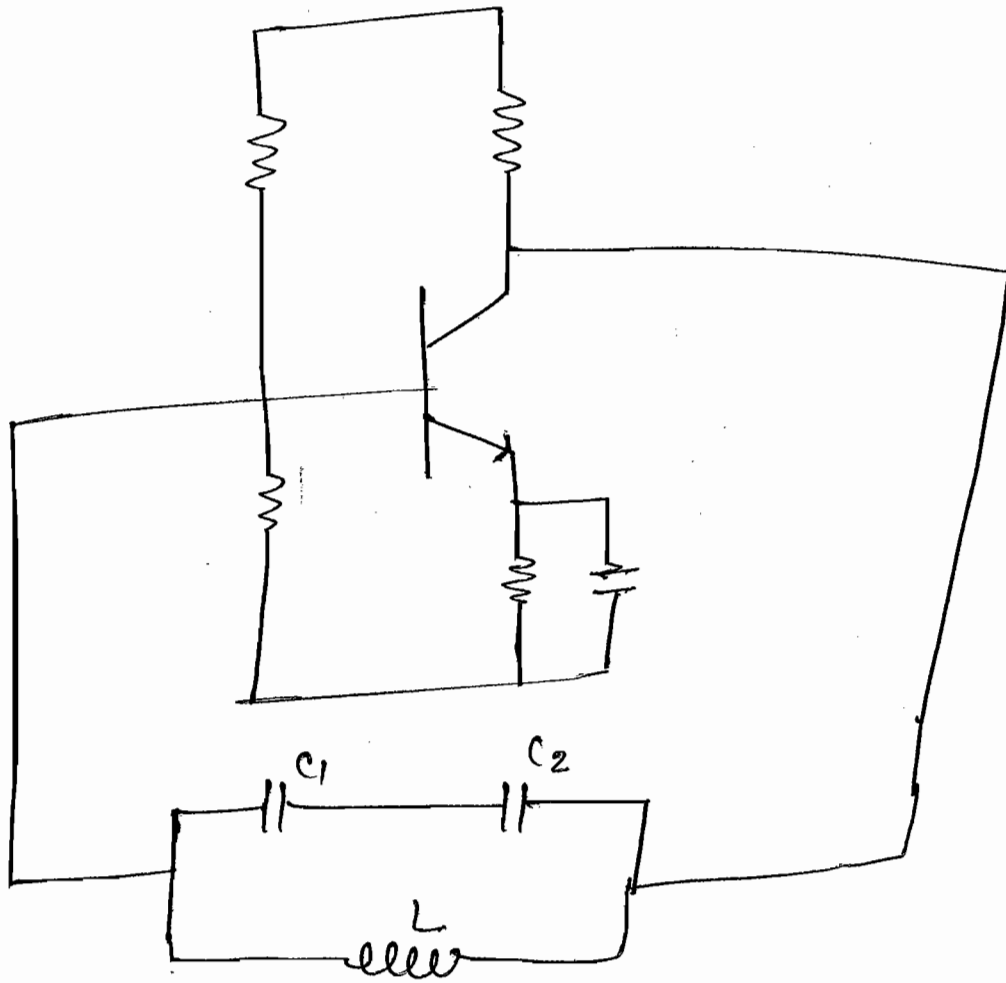

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{L} \cdot \frac{1}{C}}$$


$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{L_{eq}} \cdot \frac{1}{C_{eq}}}$$

$$f_0 = \frac{1}{2\pi} \sqrt{\left(\frac{1}{C_1} + \frac{1}{C_2}\right) \frac{1}{L}}$$

RC phase Shift	$f_0 = \frac{1}{2\pi RC \sqrt{1 + 4 \frac{R_c}{R}}}$
Hein's Bridge	$f_0 = \frac{1}{2\pi RC}$
Hearstly	$f_0 = \frac{1}{2\pi \sqrt{(L_1 + L_2)C}}$
Collpits	$f_0 = \frac{1}{2\pi \sqrt{(\frac{1}{C_1} + \frac{1}{C_2})L}}$

Net-2013  
B.A.  
Q. 05

Q. 17

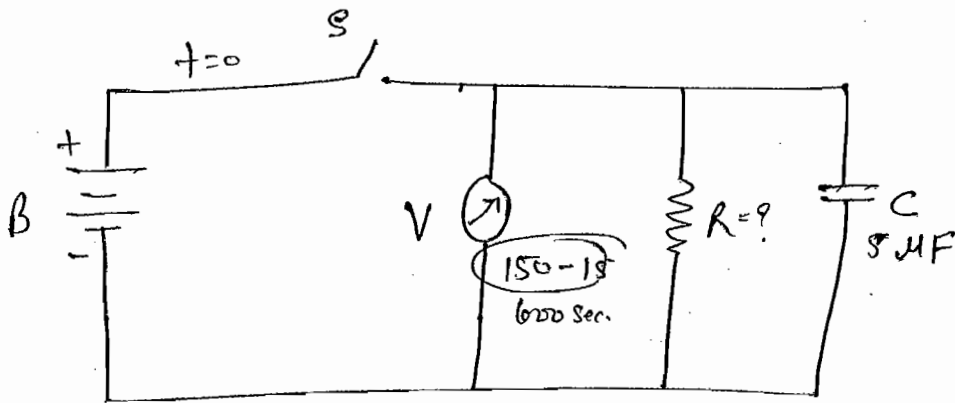

$$\omega = \frac{1}{RC}$$


$$T = \frac{1}{\omega} = RC \quad \left\{ \text{Time } \propto \frac{1}{\text{cut-off freq.}} \right\}$$

$$\boxed{T = RC}$$

$$R = \frac{1000}{5 \mu F} = 2 \times 10^5 \approx 10^5 \Omega$$

B-11  
Q.77

Sol<sup>n</sup>

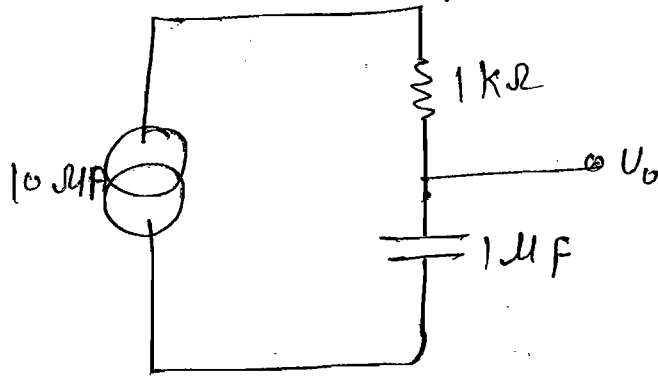

$$T = RC$$
$$= 1 \text{ k}\Omega \times 1 \mu\text{F} = 1 \times 10^{-3} = \text{1 millisecond.}$$

A

B.A.  
Q.85

Second Method

$$V = 15$$

$$T = 1000$$

$$C = 5 \mu\text{F}$$

$$R = ?$$

$$Q = CV$$

$$Q = 5 \mu\text{F} \times 15$$

$$= 75 \mu\text{C}$$

$$Q = it$$

$$i = \frac{Q}{t} = \frac{75 \mu\text{C}}{1000}$$

$$I = 75 \text{ m.A.}$$

$$R = \frac{15}{75} \times 10^9 = 2 \times 10^8 \Omega$$

## \* Consenses Theorem :-

$$Y = AB + BC + \bar{A}C$$

$$Y = AB + BC(A + \bar{A}) + \bar{A}C$$

$$= AB + ABC + \bar{A}BC + \bar{A}C$$

$$= AB[1 + C] + \bar{A}C[B + 1]$$

$$Y = AB + \bar{A}C$$

Steps:-

- ① Total no. of variable in use = 3
- ② Every variable must be repeated twice.
- ③ Select to the term which one is the compliment of other which is ans.

Q. Find the minimise expression  $Y = AB + \bar{B}C + AC$

Sol<sup>n</sup>

$$Y = AB + \bar{B}C$$

Q.

$$Y = AB + \bar{B}C + AC$$

Sol<sup>n</sup>

$$Y = \bar{B}C + AC$$

Q.

$$Y = \bar{A}\bar{B} + \bar{B}\bar{C} + \bar{A}\bar{C}$$

Sol<sup>n</sup>

$$Y = \bar{A}\bar{B} + \bar{A}\bar{C} \quad \text{Ans}$$



Q.  $Y = AB + \bar{A}C + B\bar{C}$

Soln  

$$Y = AB + \bar{A}C$$

Q.  $Y = (A+B)(B+C)(\bar{A}+C)$

Soln  

$$Y = (\bar{A}+B)(\bar{A}+C)$$


Q.  $Y = (\bar{x} + \bar{y})(\bar{y} + \bar{z})(x + \bar{z})$

Soln  


$$Y = (\bar{x} + \bar{y})(x + \bar{z})$$
 Ans

D.V.  
Q. The current gain in the transistor  $\beta = 100$   
the value of collector current  $I_c$  is?

(a)

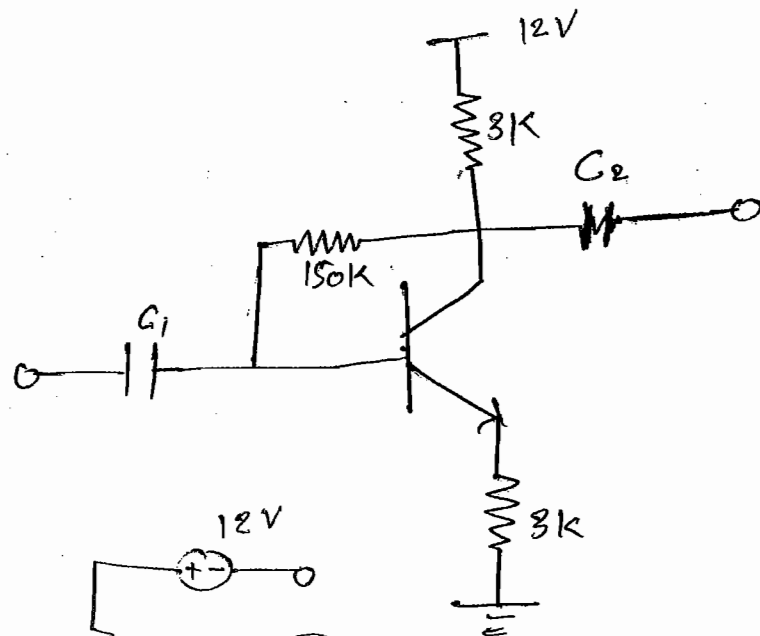

Soln

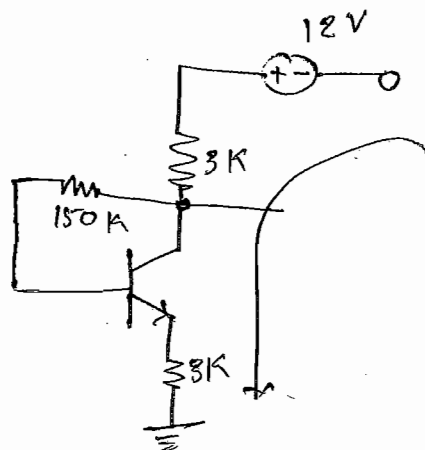

$$-12 + (I_E + I_B) 3k + I_B \times 150k + V_{BE} + I_E \times 3k = 0$$

$$(I_E + I_B) 3k + I_B 150k + (I_B + I_C) 3k = 11.3$$

$$I_C 3k + I_B 3k + I_B 150k + I_B 3k + I_C 3k = 11.3$$

$$I_C 6k + I_B 156k = 11.3$$

$$\beta I_B 6k + I_B 156k = 11.3$$

$$100 \times 6k I_B + 156k I_B = 11.3$$

$$756 I_B = 11.3$$

$$I_B = \frac{11.3}{756} = 0.014 \text{ m.A.}$$

$$I_C = \beta I_B$$

$$= 100 \times 0.014 \text{ m.A.}$$

$$= 1.4 \text{ m.A. } \underline{\underline{Ans}}$$

Q. In order to measure a maximum of 1V with a resolution of 1 millivolt using n-bit analog to digital converter determine n-bit?

Sol<sup>n</sup>

resolution = 1 m.V

$$V_r = 1V$$

$$\text{reso} = \frac{V_r}{2^n - 1}$$

$$\Rightarrow 1 \text{ m.V.} = \frac{1}{2^n - 1}$$

$$2^n - 1 = \frac{1}{1 \text{ m.V.}}$$

$$2^{11} - 1 = 1000$$

$$2^n = 1001$$

$$2^n \approx 2^{10}$$

$$\boxed{n = 10}$$

Q. A low pass filter formed by simple R-C circuit at the cut-off angular frequency. the voltage gain and the phase of output voltage relative to input voltage respectively are -


(a)  $0.71 \angle +95^\circ$

(b)  $0.71, -95^\circ$

(c)  $0.5 \angle -90$

(d)  $0.5 \angle +90^\circ$

Sol<sup>n</sup>

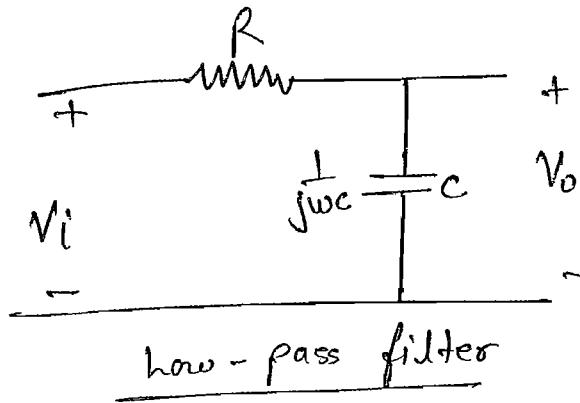

$$V_o = \frac{V_i \times \frac{1}{j\omega C}}{R + \frac{1}{j\omega C}}$$

$$\frac{V_o}{V_i} = \frac{\frac{1}{j\omega C}}{R + \frac{1}{j\omega C}} = \frac{1}{1 + j\omega RC}$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1 + \omega^2 R^2 C^2}} = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$
$$= \frac{1}{\sqrt{1 + \left(\frac{\omega}{\frac{1}{RC}}\right)^2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

$$\omega = \omega_G$$

$$\left| \frac{V_o}{V_i} \right| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707$$

$$\frac{V_o}{V_i} = \frac{1}{1+j\omega RC}$$


$$\angle \frac{V_o}{V_i} = -\tan^{-1}(\omega RC) = -\tan^{-1}\left(\frac{\omega}{\frac{1}{RC}}\right)$$

$$= -\tan^{-1}\left(\frac{\omega}{\omega_c}\right) = -\tan^{-1}\left(\frac{\omega}{\omega}\right)$$

$$= -\tan^{-1}(1) = -\tan^{-1}(\tan 45^\circ)$$

$$= \underline{\underline{-90^\circ}} \quad \underline{\underline{\text{Ans}}}$$


Digital  
B.A.  
(1)

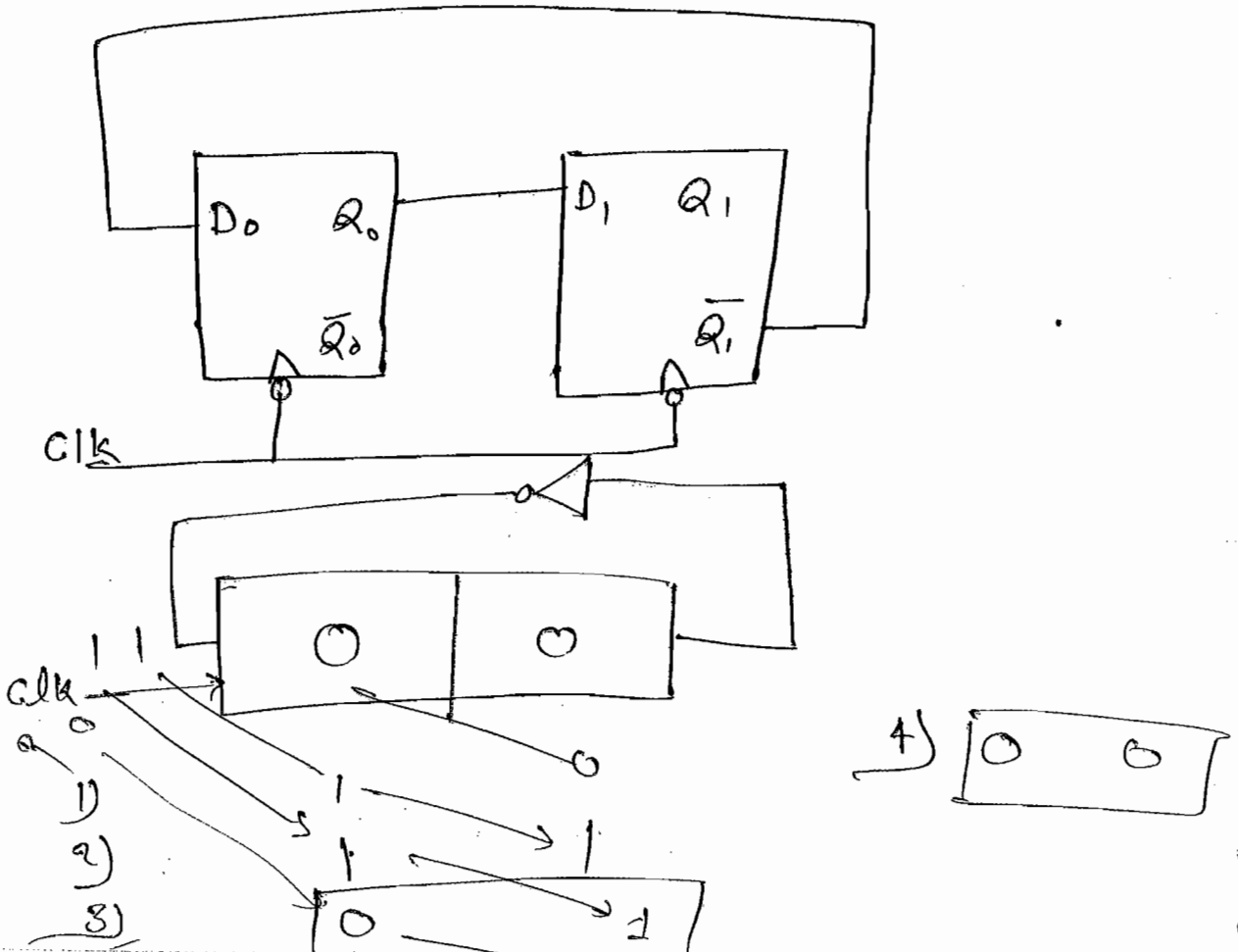

~~335~~ OP.


$$4 \overline{) 335} \\ \underline{37} \\ 15 \\ \underline{12} \\ 3 \rightarrow$$

2

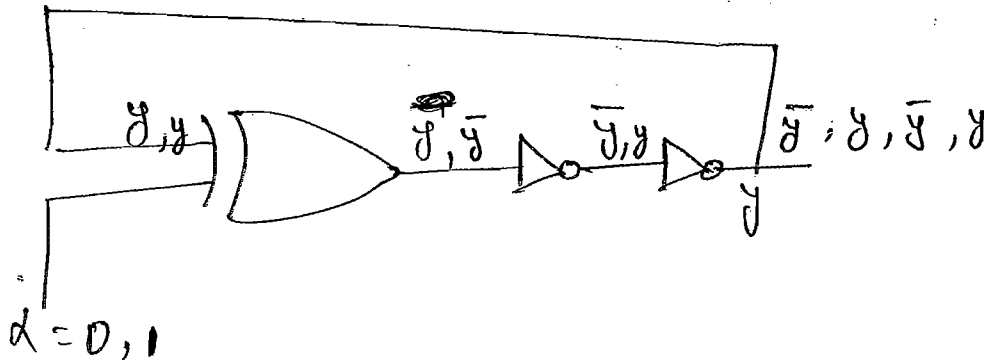

So  $X=1$

3

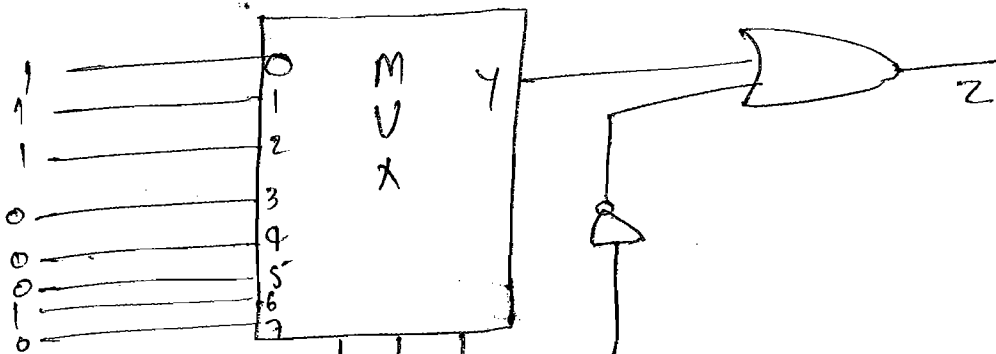

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

$$\bar{A}\bar{B}\bar{C} \cdot 1 + \bar{A}\bar{B}C \cdot 1 + \bar{A}B\bar{C} \cdot 1 + AB\bar{C} \cdot 1 = Z$$


$$Z = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + AB\bar{C} + \bar{C}$$

$$= \bar{A}\bar{B} + \bar{A}B\bar{C} + AB\bar{C} + \bar{C}$$

$$= \bar{A}\bar{B} + \bar{C} [1 + AB + \bar{A}B]$$

$$Z = \bar{A}\bar{B} + \bar{C}$$

4

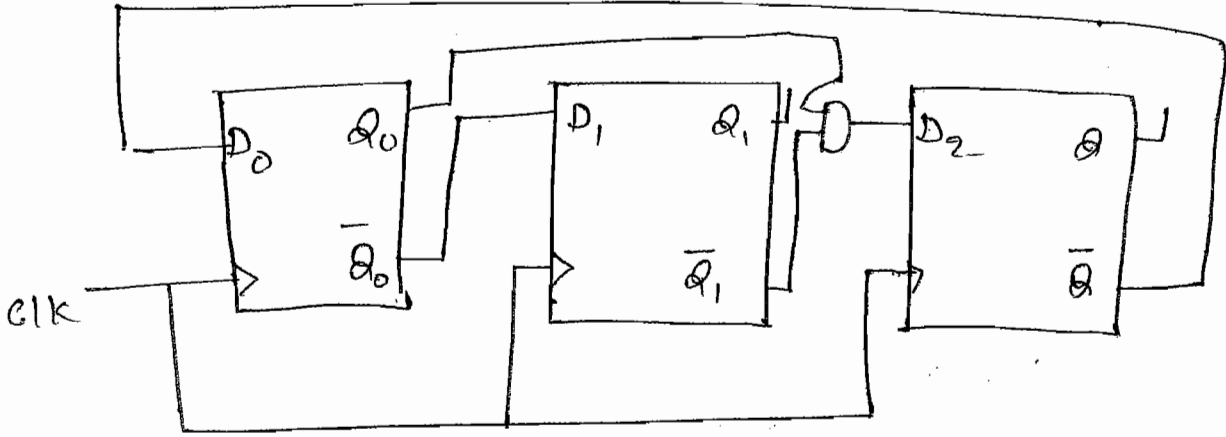

$$D_1 = \bar{Q}_0$$


$$D_0 = \bar{Q}_2$$

$$D_2 = \bar{Q}_0 \bar{Q}_1$$

	$D_0$	$D_1$	$D_2$	$Q_0$	$Q_1$	$Q_2$
X	1	1	0	0	0	0
1)	1	0	0	1	1	0
2)	1	0	1	1	0	0
3)	0	0	1	1	0	1
4)	0	1	0	0	0	1
5)	1	1	0	0	1	0
				1	1	0

mod - 5

5

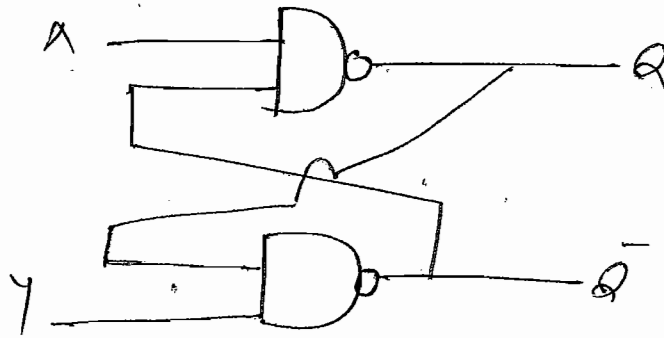


$X=0, Y=0$  invalid (a)

6

	AB	00	01	11	10
c	1	1	1	X	0
0	0	0	0	X	0

$$Y = C\bar{A}$$


Q. Identify the flip-flop.

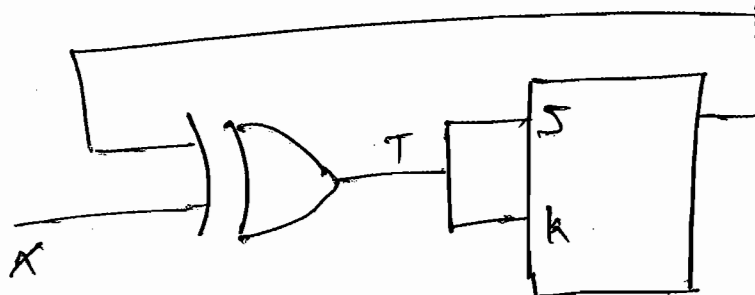

$$T = a_1 \oplus Q$$



So  $a_1 = D$

Q. Identify

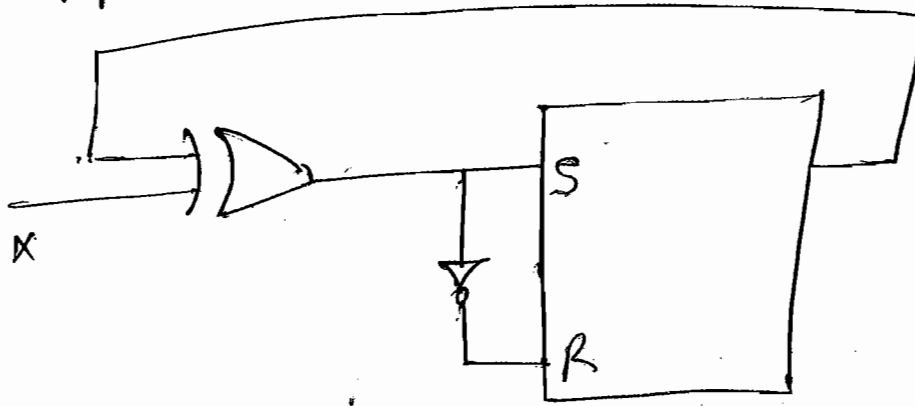

T-flip-flop.

Q.9

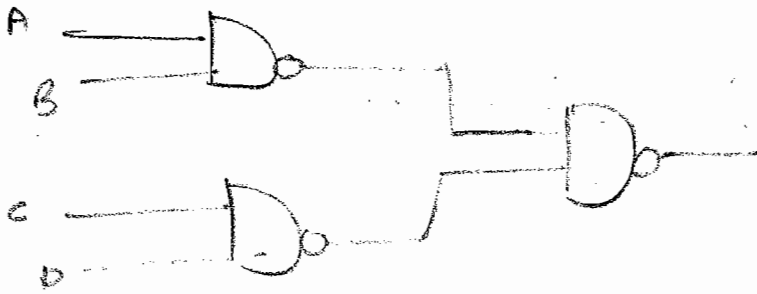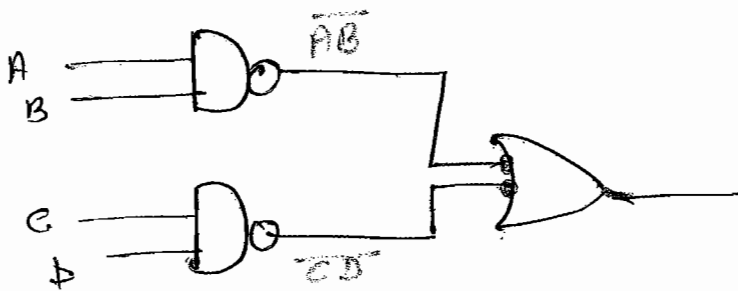

∴ min<sup>m</sup> no. of nand gate required = 3.



~~\* fix~~

# \* Flip-Flop Conversion :-

Steps -

- (i) Identify the flip-flop which is required.
- (ii) Draw the characteristic table.
- (iii) Develop the excitation table for the ~~required~~ <sup>given</sup> flip-flop. Minimise by k-map.
- (iv) Implement by logic gates.

## (i) Convert JK to T-flip-flop :-

T	$Q_n$	$Q_{n+1}$	JK
0	0	0	0 X
0	1	1	X 0
1	0	1	1 X
1	1	0	X 1

$Q_n$	$Q_{n+1}$	SR
0	0	0 X
0	1	1 0
1	0	0 1
1	1	X 0


T	$Q_n$	0	1
0	0	0	X
1	0	1	X

$J = T$

T	$Q_n$	0	1
0	0	X	0
1	0	X	1

$K = T$

JK
0 X
1 X
X 1
X 0

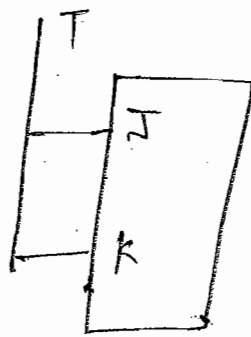

T-flip-flop

\* Convert JK to  $\oplus$  flip-flop :-


D	$Q_n$	$Q_{n+1}$	JK
0	0	0	0 X
0	1	0	X 1
1	0	1	1 X
1	1	1	X 0

$Q_n$	0	1
D	0	X
1	1	X

$$J = D$$

$Q_n$	0	1
D	X	1
1	X	0

$$K = \bar{D}$$

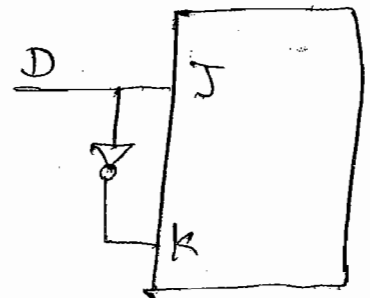

\* Convert D to T flip-flop :-

T	$Q_n$	$Q_{n+1}$	D ( $= Q_{n+1}$ )
0	0	0	0
0	1	1	1
1	0	1	1
1	1	0	0

	$Q_n$	0	1
T	0	0	1
	1	1	0

$$D = \bar{T}Q_n + T\bar{Q}_n$$

$$D = T \oplus Q_n$$

or

$$T = D \oplus Q_n$$

\* Point To be remember :-

$$JK \longrightarrow T$$

$$J = T$$

$$K = T$$

$$JK \longrightarrow D$$

$$J = D$$

$$K = \overline{D}$$

$$SR \longrightarrow D$$

$$S = D$$

$$R = \overline{D}$$

$$D \longrightarrow T$$

$$D = T \oplus Q_n$$



$$T \longrightarrow D$$

$$T = D \oplus Q_n$$

# \* Steps for identification

- ① Draw the circuit diagram by using ordinary gate
- ② Substitute bubble in front of AND gate and input of OR gate so that bubble is balanced.
- ③ Replace every gate by Nand gate, it gives min<sup>m</sup> no. of nand gate.


Ex -

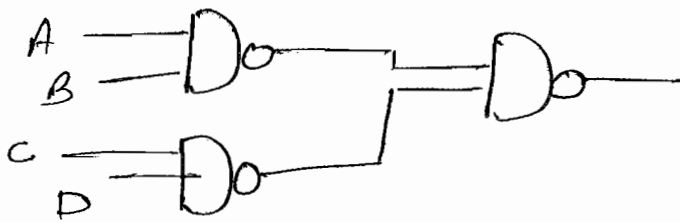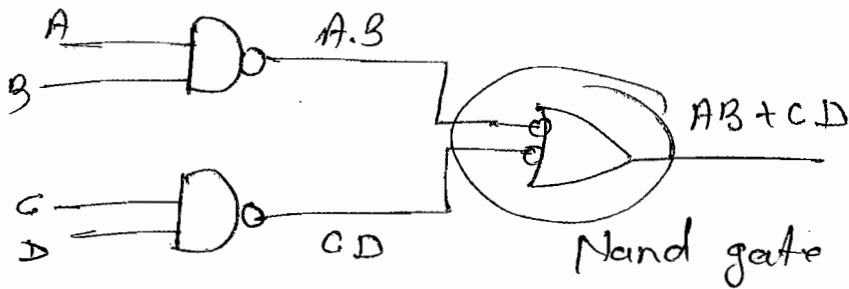


= ③

Q.




$$y = AB + CD + E$$

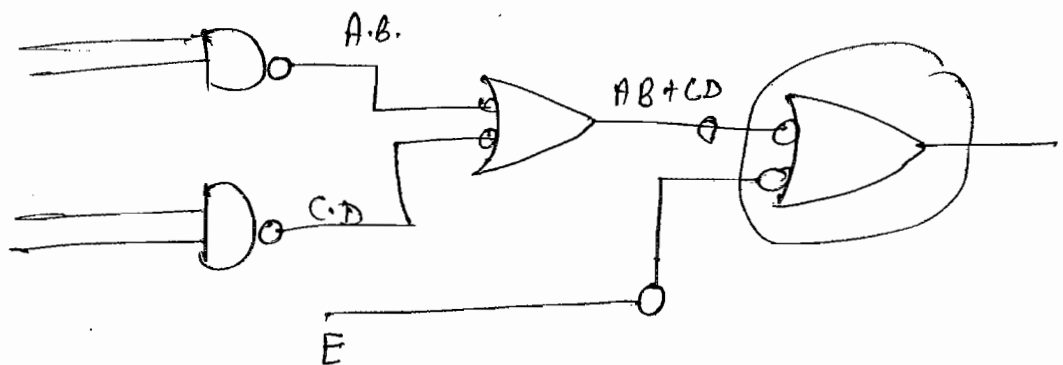

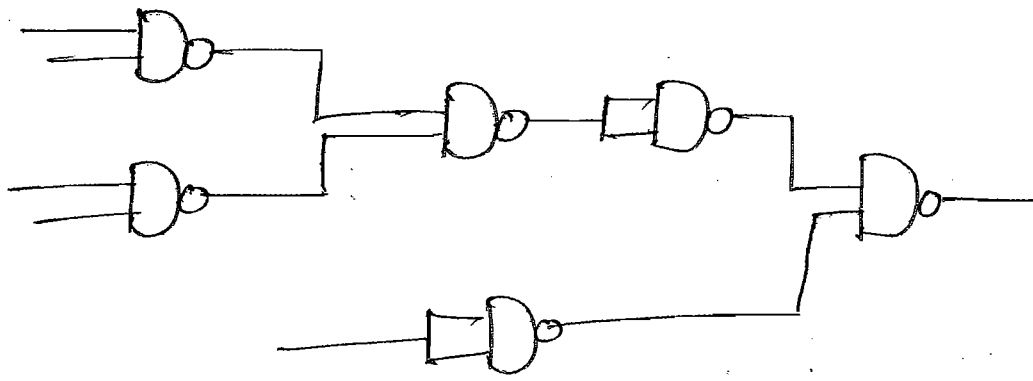

118.



$$Y = AB + CD + \bar{E}$$

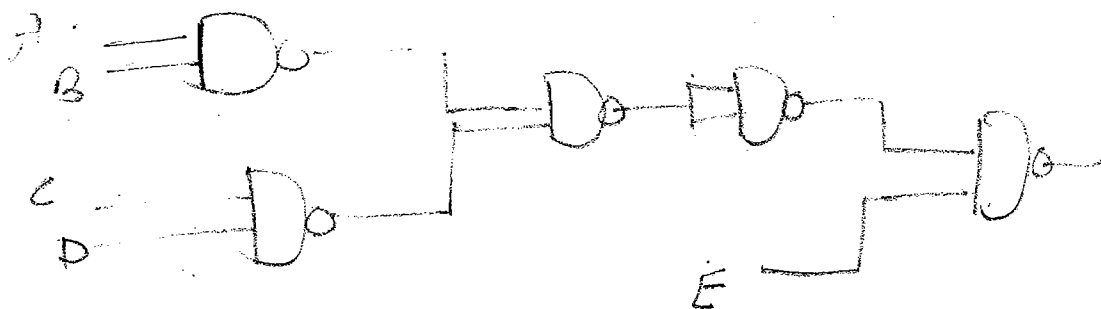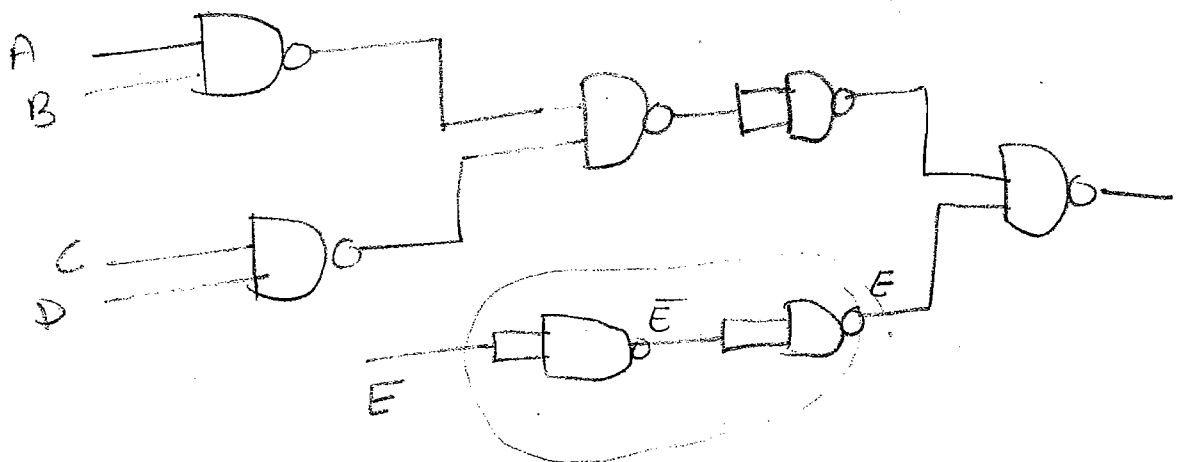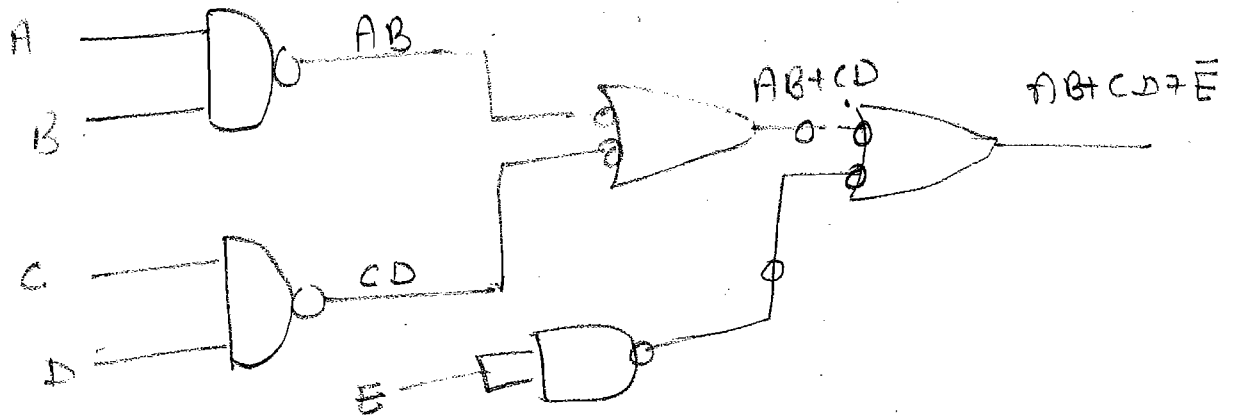

\* Steps for identification minimum no. of Nor gate.  $\Rightarrow$


- ① Draw the circuit diagram by using ordinary gates.
- ② Substitute bubble at the infront of OR-gate and at the input of AND-gate.
- ③ Replace every gate by NOR-gate it will give minimum no. of nor gate.

Q. 9

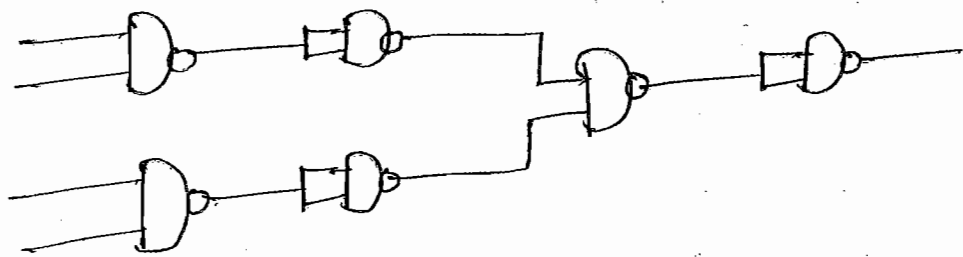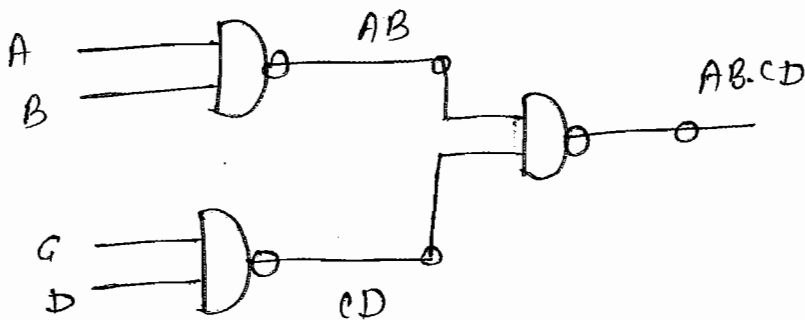


= 6 Ans

Q. 11

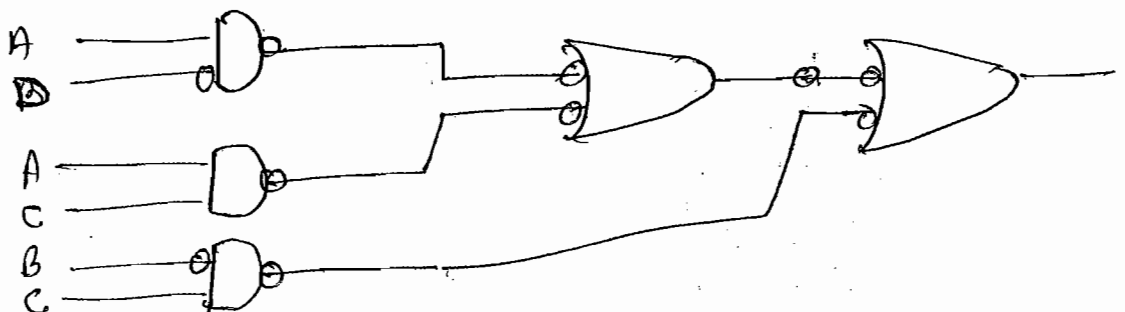

12

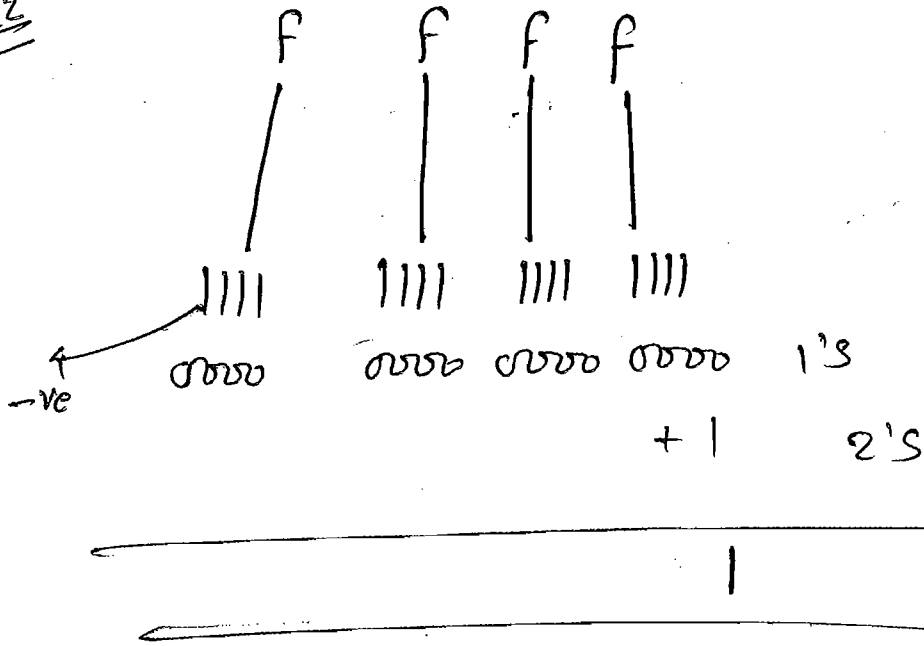


13

	6	0000	
36 →	5	0001	→ <u>Ans</u>
35	4	0010	
33	3	0011	
34	2	0100	
33	1	0101	
32   6 →	0	0110	
	15	0111	
	14	1000	
	13	1001	
	12	1010	
	11	1011	
	10	1100	
	9	1101	
	8	1110	
	7	1111	



14

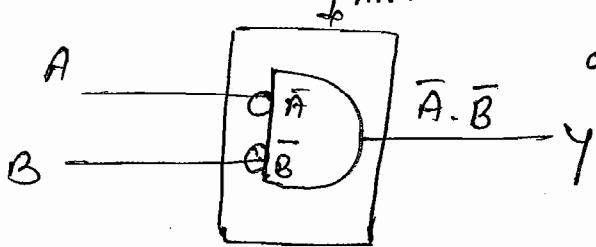

duality -

$$\overline{A \cdot B} \uparrow \text{OR} \overline{A} + \overline{B}$$

-ve logic

for +ve logic

$$Y = \overline{A} + \overline{B} \leftarrow \text{OR - Gate}$$


15

$$f(A, B, C, D, E) = C + \overline{D}E$$


A	B	C	D	E
0	0	0	0	0
0	0	0	0	1
0	0	1	0	0
0	0	1	0	1
0	1	0	0	0
0	1	0	0	1
0	1	1	0	0
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1
1	1	0	0	0
1	1	0	0	1
1	1	0	1	0
1	1	0	1	1

= 4

18

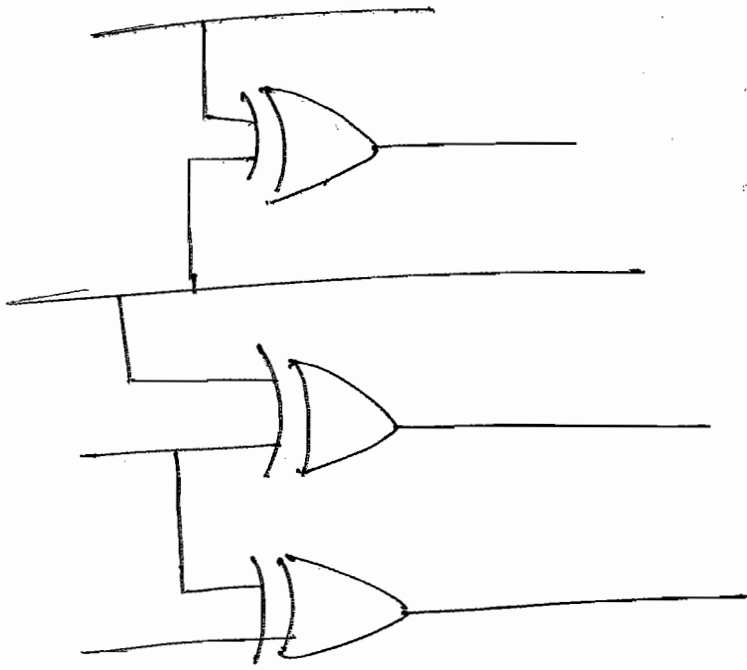


23

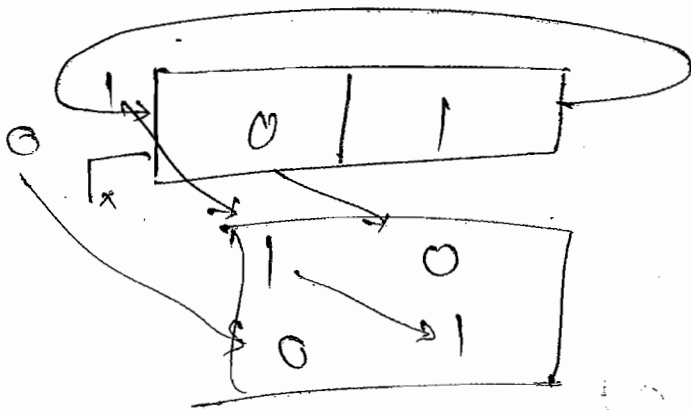

mod 2 Counter

22


$$4 = 2^2 = 16$$

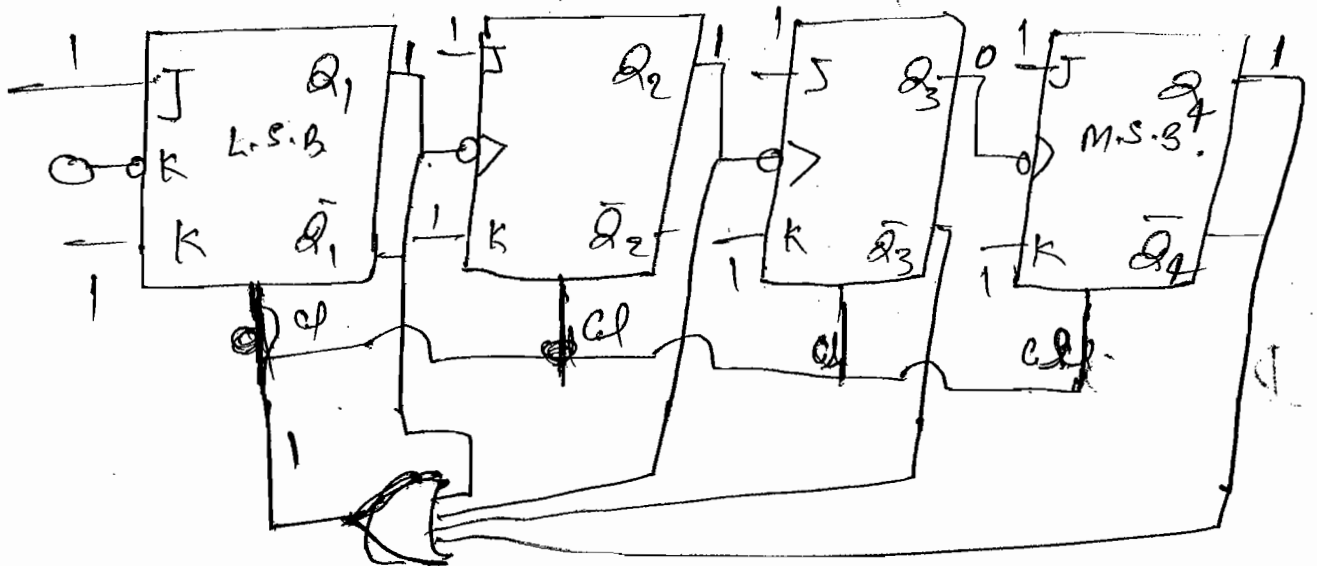

$Q_4$	$Q_3$	$Q_2$	$Q_1$
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0


1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1

Q For the given circuit diagram. Identify the ~~gate~~ mod.

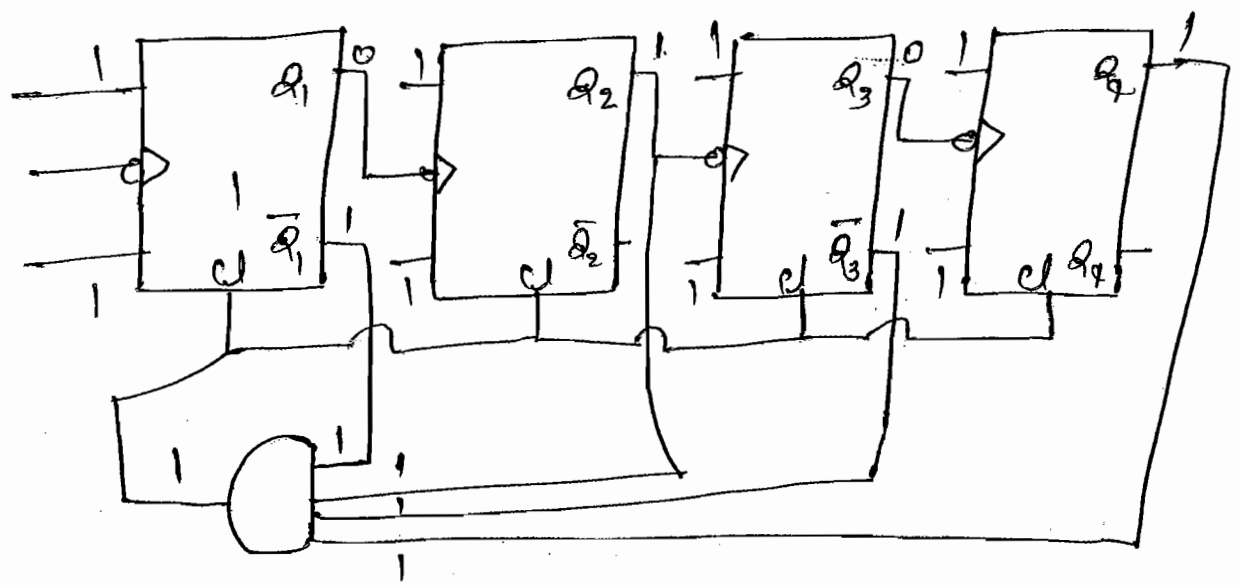


mod 10 -

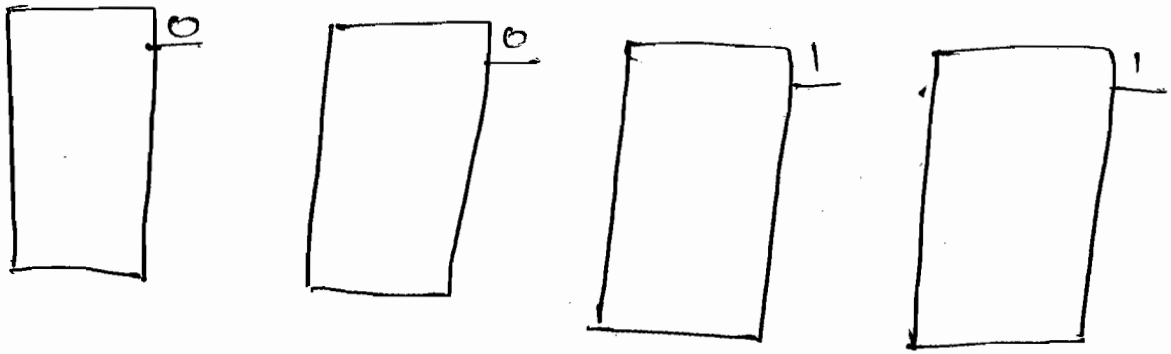Q. Draw the circuit diagram for mael - 12 up counted by using all four inputs.



Q.16

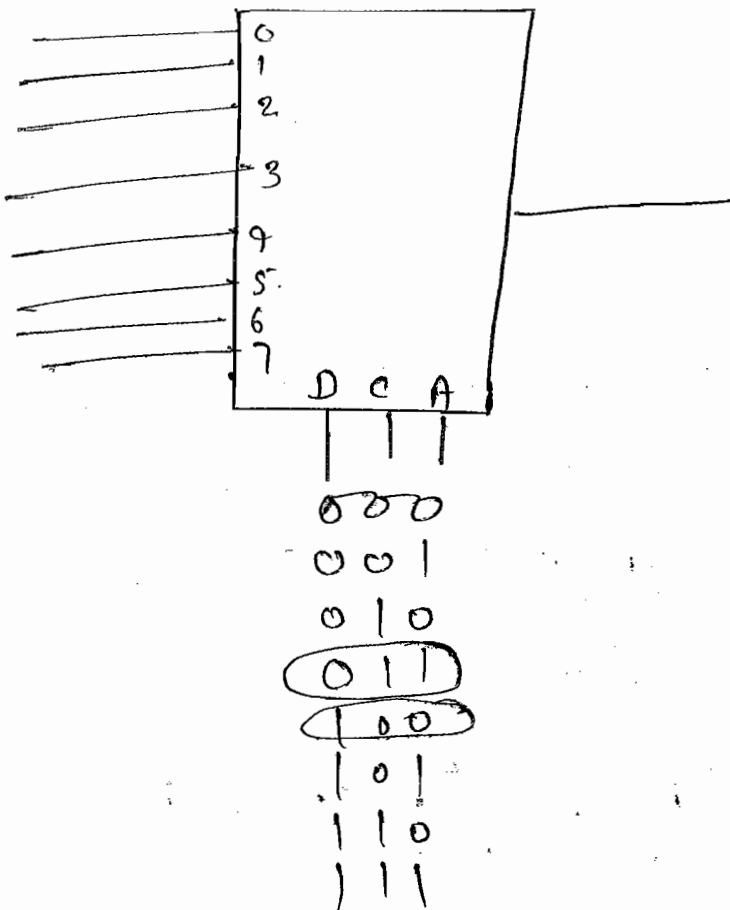

A	B	C	D	
0	0	0	0	
0	0	0	1	0
0	0	1	0	
0	0	1	1	
0	1	0	0	
0	1	0	1	0
0	1	1	0	
0	1	1	1	
1	0	0	0	
1	0	0	1	
1	0	1	0	1
1	0	1	1	1
1	1	0	0	
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

$$f(A, B, C, D) = AC + A\bar{B}D + A\bar{C}D$$



27

$(7E)_H$  &  $(8F)_H$

$\rightarrow 01111110$   
 $\rightarrow + 01011111$

$\underline{00100001}$   
2

EXOR


00010000

00000000

$00000000$   
 $00000000$   
 $00000000$   
 $00100001$

00100001

39

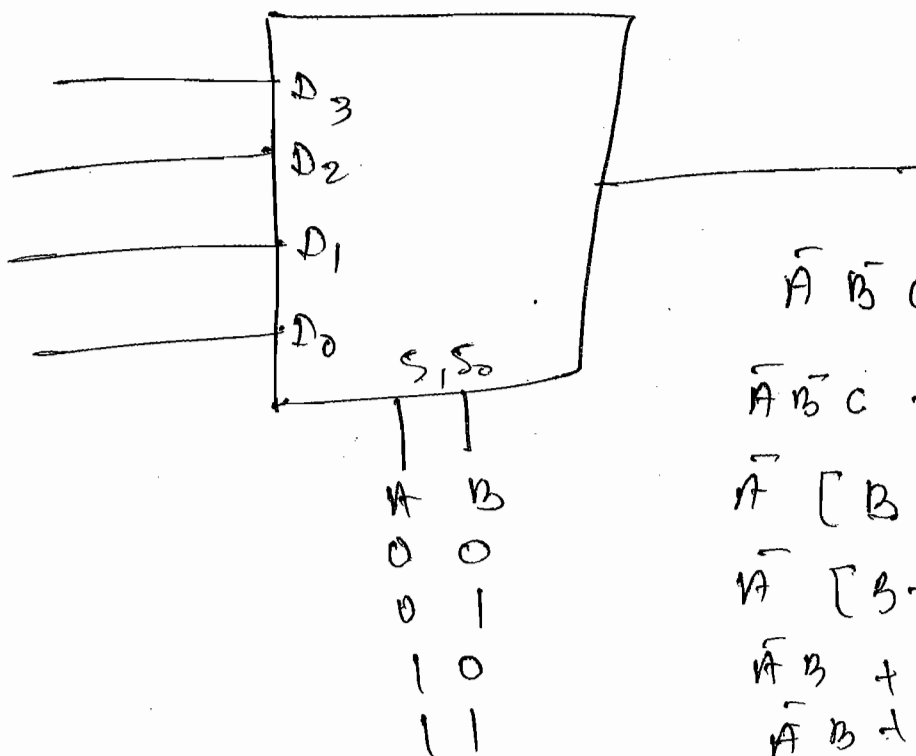

$$\bar{A}\bar{B}C + \bar{A}B + A\bar{B} + AB$$

$$\bar{A}\bar{B}C + \bar{A}B + A\bar{B} + AB$$

$$\bar{A} [B + \bar{B}C] + A [B + B]$$

$$\bar{A} [B + C] + A$$


$$\bar{A}B + \bar{A}C + A$$

$$\bar{A}B + \bar{A}C + A$$

$$\bar{A}B + A + C$$

$A + B + C$

Q. 35

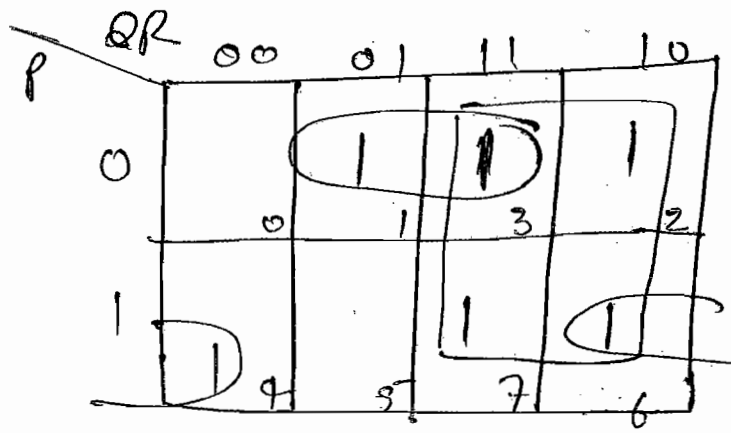


$$= \bar{P}R + P\bar{R} + Q$$

$$= P \oplus R + Q$$


one XOR and 1 OR

38) 15-bit (d)

39)

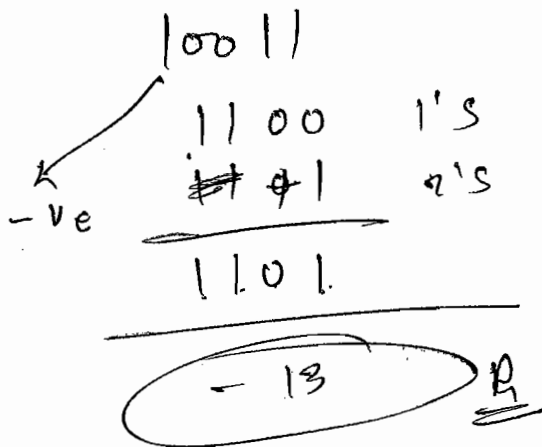


40)

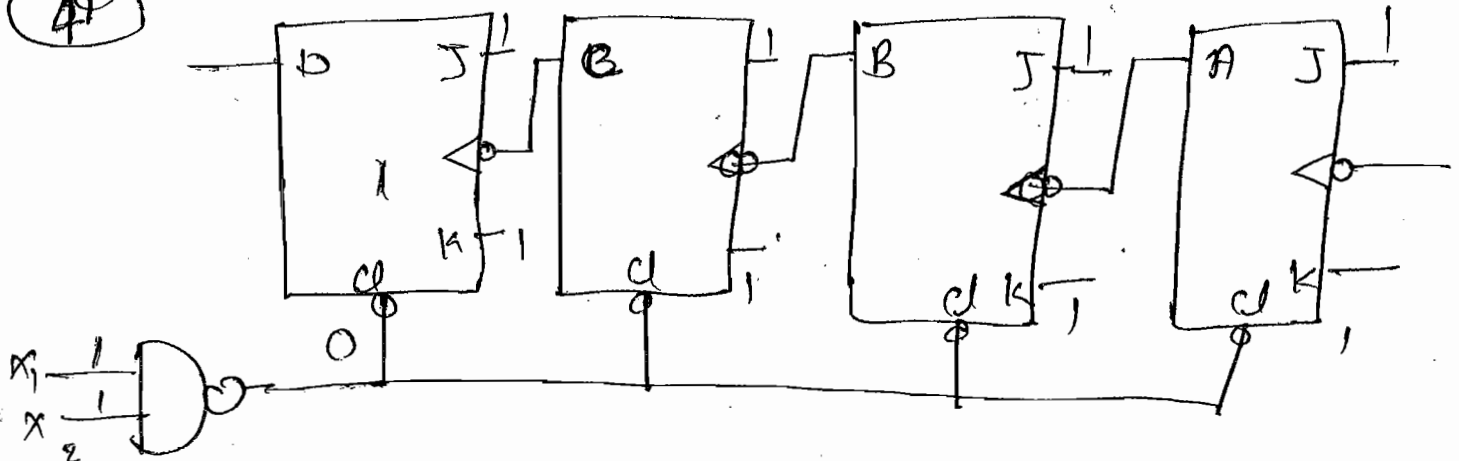

0000  
 0001  
 0010  
 0011  
 0100  
 0101  
 0110  
 0111  
 1000  
 1001  
 1010  
 1011  
1100  
 1101  
 1110  
 1111


46

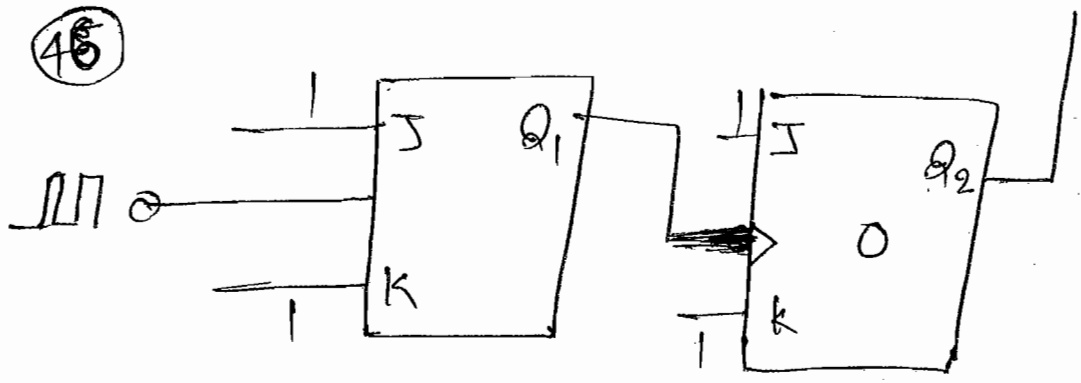

	$Q_2$ MSB	$Q_1$ LSB
4	0	0
3	0	1
2	1	0
1	1	1

↑  $Q$   
 ← Ans


47

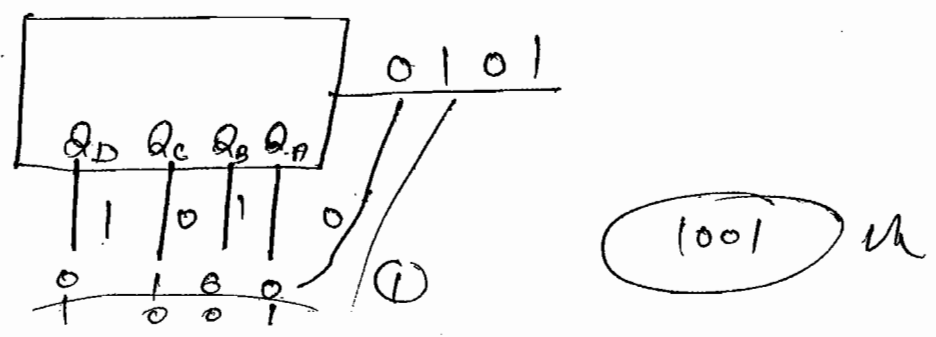



# \* Resonance $\rightarrow$

Series RLC Network:-

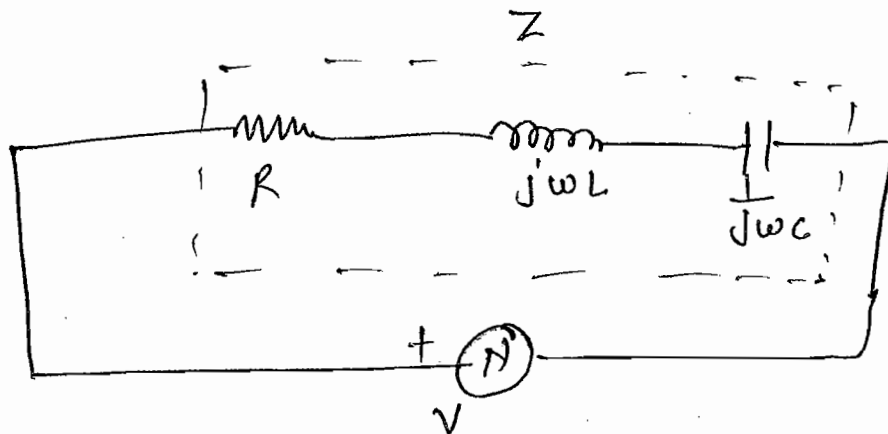

$$Z = R + j\omega L + \frac{1}{j\omega C}$$

$$= R + j\omega L - \frac{1}{\omega C}$$

$$= R + j\left(\omega L - \frac{1}{\omega C}\right)$$

$$|Z| = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

At resonance  
~~Series~~

$$\omega L = \frac{1}{\omega C}$$


$$Z = \sqrt{R^2}$$

$$\boxed{Z_{\min} = R_{\min}}$$

$$I = \frac{V}{Z}$$

$$\boxed{I = \frac{V}{R_{\min}}} \leftarrow \text{maximum}$$


$I_{\max}$  at resonance freq.

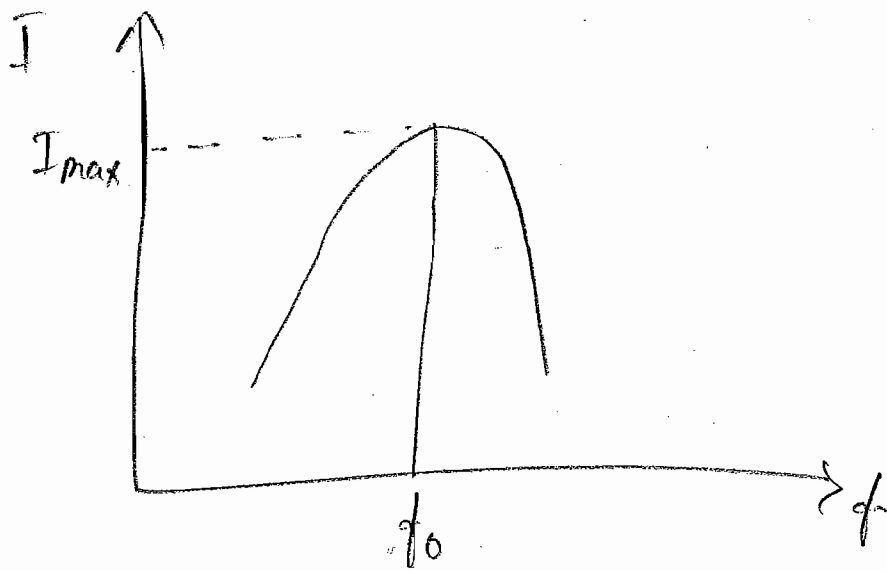

$$Z = \sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}$$
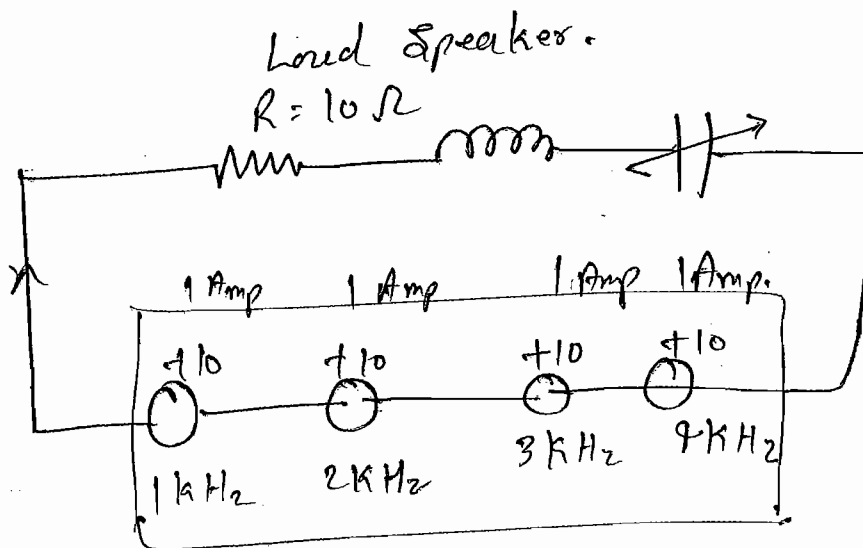
### Use of Resonance :-


It is used to select only a single frequency by neglecting all other frequencies.



To calculate the resonance freq. of any circuit, equate imaginary component of impedance expression to zero.

Q. For the given circuit diagram determine the resonance frequency.

Sol<sup>n</sup>

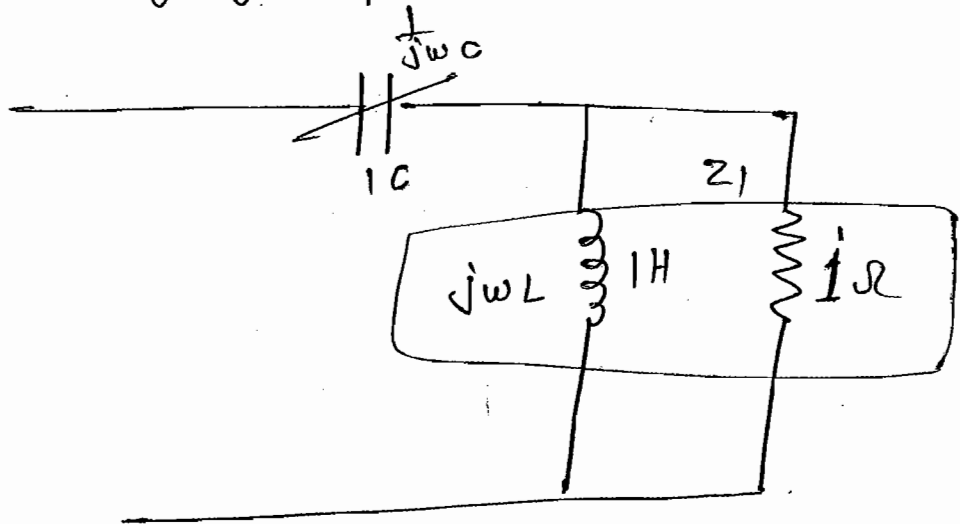

$$Z_1 = \frac{1 \times j\omega}{1 + j\omega}$$

So  $Z = Z_1 + \frac{1}{j\omega c}$

$$= \frac{j\omega}{1 + j\omega} + \frac{1}{j\omega} = \frac{(j\omega)^2 + 1 + j\omega}{j\omega(1 + j\omega)}$$

$$= \frac{1 + j\omega - \omega^2}{j\omega(1 + j\omega)}$$

$$= \frac{-j(1 - \omega^2) + j\omega}{\omega(1 + j\omega)}$$

$$= \frac{-j(1 - \omega^2) + j\omega(1 - j\omega)}{\omega(1 + j\omega)(1 - j\omega)}$$

$$= \frac{j[(1 - \omega^2) + j\omega - j\omega(1 - \omega^2) + \omega^2]}{\omega(1 + \omega^2)}$$


$$\begin{aligned}
 &= \frac{-j(1-\omega^2) + \omega - \omega(1-\omega^2) - j\omega^2}{\omega(1+\omega^2)} \\
 &= \frac{\omega - \omega(1-\omega^2) - j[1-\omega^2 + \omega^2]}{\omega(1+\omega^2)} \\
 &= \frac{\omega - \omega(1-\omega^2) - j}{\omega(1+\omega^2)} \\
 &= \frac{\omega - \omega(1-\omega^2)}{\omega(1+\omega^2)} - \frac{j}{\omega(1+\omega^2)}
 \end{aligned}$$

$$\text{So } \frac{-1}{\omega(1+\omega^2)} = 0$$

$-1 \neq 0$  not possible

So resonant freq. does not exist.

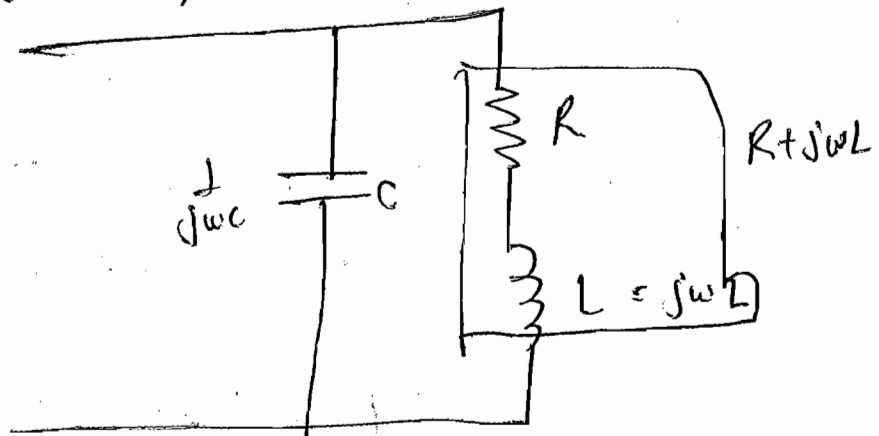Q. for the given circuit diagram calculate given frequency. (Resonance).



for simplicity

$$\text{Conductance} = j\omega C + \frac{1}{R + j\omega L} \quad (1)$$

$$= \frac{j\omega c [R + j\omega L] + 1}{(R + j\omega L)(R - j\omega L)}$$

$$= \frac{[j\omega c [R + j\omega L] + 1] [R - j\omega L]}{R^2 + \omega^2 L^2}$$

$$= \frac{j\omega R c [R + j\omega L] + R + \omega^2 L c (1 + j\omega L) - j\omega}{(R^2 + \omega^2 L^2)}$$

$$= \frac{j\omega R^2 c - \omega^2 R c + R + \omega^2 R L c + j\omega^2 L^2 c - j\omega}{R^2 + (\omega L)^2}$$

equating imaginary part to zero.

$$\frac{j[\omega R^2 c + \omega^2 L^2 c - \omega L]}{R^2 + (\omega L)^2} = 0$$

$$\frac{R^2 c + \omega^2 L^2 c - L}{R^2 + (\omega L)^2} = 0$$

$$R^2 c + \omega^2 L^2 c - L = 0$$

$$\omega^2 L^2 c = L - R^2 c$$


$$\omega^2 = \frac{L - R^2 c}{L^2 c} = \frac{R^2 c}{L^2 c}$$

$$\boxed{\omega = \sqrt{\frac{1}{Lc} - \frac{R^2}{L^2}}}$$

Ans

Q. Calculate the resonance freq.

- (a) 1.41
- (b) 1
- (c) 2
- (d) 1.73

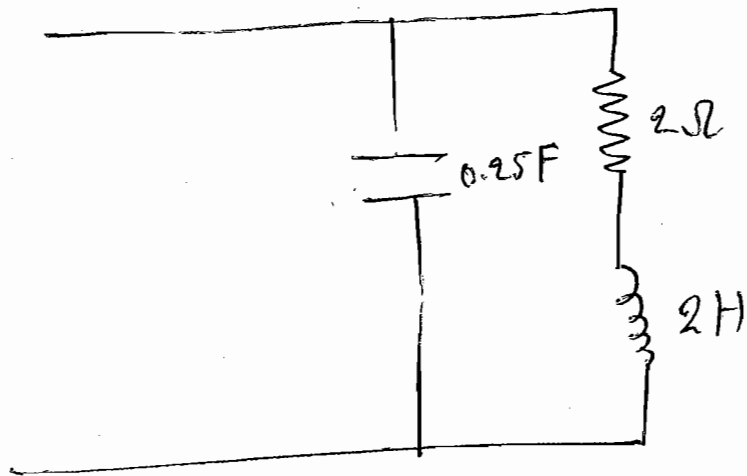



Sol<sup>n</sup>

Normal  $\omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{2 \times 0.25}} = 1.41$


But it is not right

$\omega = \sqrt{\frac{1}{LC} - \frac{R^2}{C^2}} = 1$



Digital  
(68)

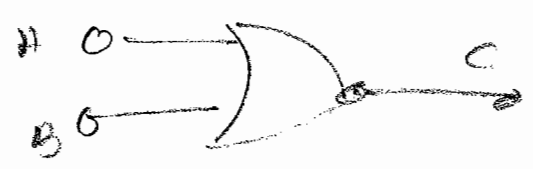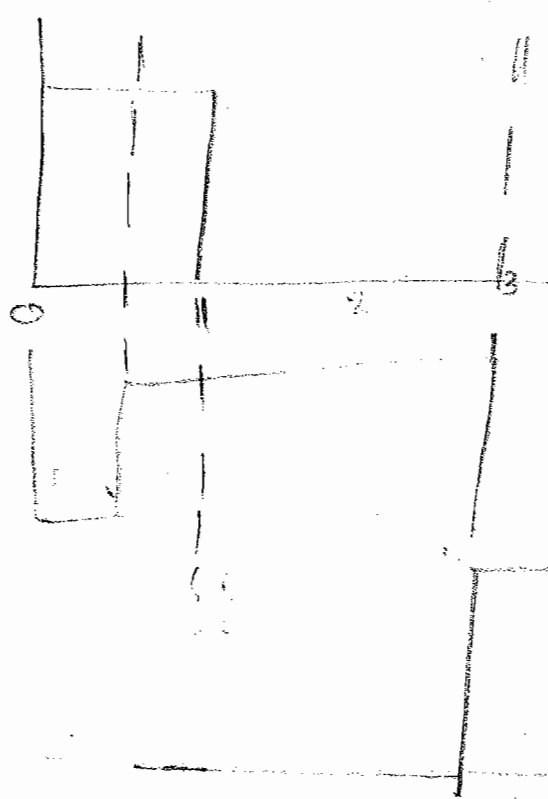

81

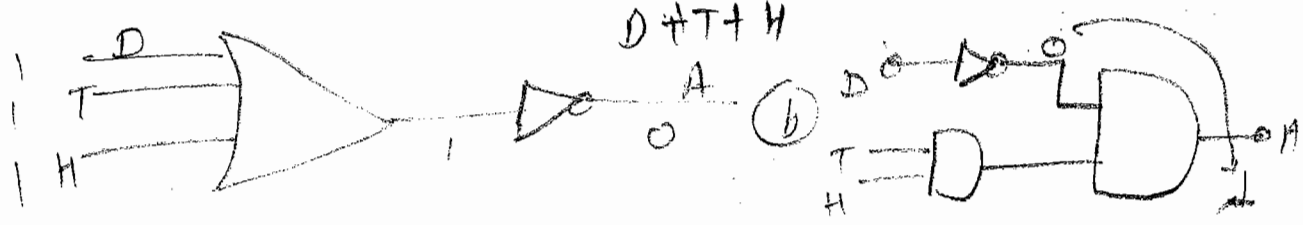

82

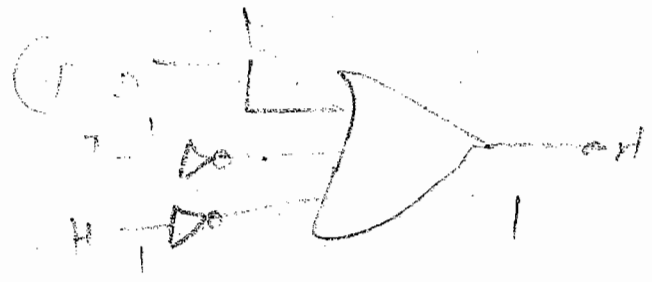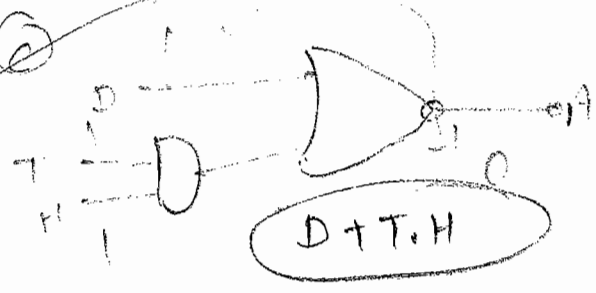

T → 1, < a

A = 0

H → 1, < a

D = 1 ← one the clear


D as T and humidity

1 1 1 → A = 0

D + T.H


82 a

# \* Half - Wave Rectifier :-

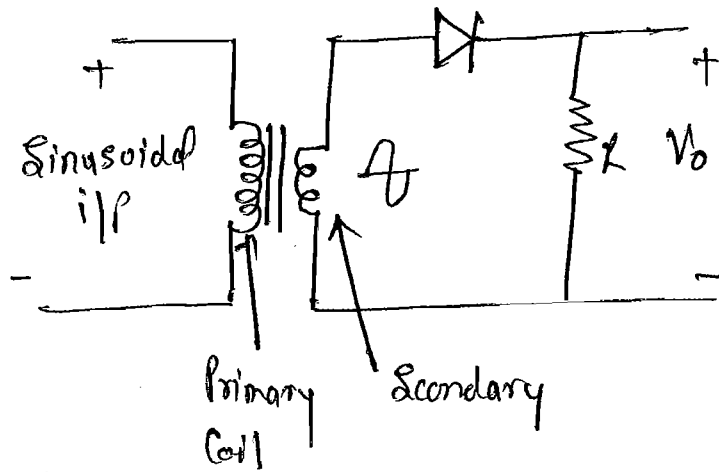

Step-up transformer increases the amplitude of applied i/p and reproduces at secondary of the transformer.

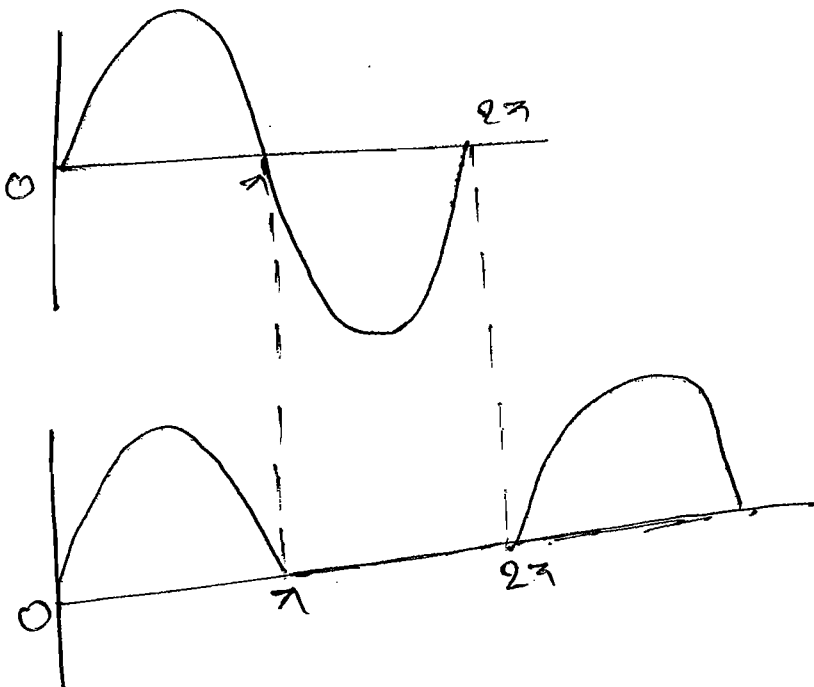If the applied i/p whose amplitude is decrease, it called as step down transformer.



\* D.C. Value or Average value :-

$$= \frac{1}{2\pi} \int_0^{2\pi} f(x) dx$$

$$= \frac{1}{2\pi} \int_0^{2\pi} V_m \sin(x) dx.$$



$$= \frac{1}{2\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega + \frac{1}{2\pi} \int_{\pi}^{2\pi} 0 \, d\omega$$

$$= \frac{V_m}{2\pi} \int_0^{\pi} \sin \omega t \, d\omega = \frac{V_m}{2\pi} [-\cos \omega]_0^{\pi}$$

$$= \frac{V_m}{\pi}$$

So Average value of halfwave rectifier =  $\frac{V_m}{\pi}$

# Average value of Full wave Rectifier :-  
dc value

$$= \frac{2V_m}{\pi}$$

\* Root mean Square Value :-

Power is also called as mean square value of function.

$$= \sqrt{\frac{1}{2\pi} \int_0^{2\pi} f(x) \, dx}$$

$$= \sqrt{\frac{1}{2\pi} \left[ \int_0^{\pi} f(x) \, dx + \int_{\pi}^{2\pi} f(x) \, dx \right]}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{\pi} (V_m \sin \omega)^2 \, d\omega}$$

$$= \sqrt{\frac{1}{2\pi} \int_0^{\pi} V_m^2 \sin^2 \omega \, d\omega}$$

$$= V_m \sqrt{\frac{1}{2\pi} \int_0^{2\pi} \sin^2 \omega t \, d\omega}$$

$$= \frac{V_m}{2} \sqrt{\frac{1}{\pi} \int_0^{2\pi} 1 - \cos 2\omega \, d\omega}$$

$$= \frac{V_m}{2} \sqrt{\frac{1}{\pi} \left[ \omega - \frac{\sin 2\omega}{2} \right]_0^{2\pi}}$$

$$= \frac{V_m}{2} \sqrt{\frac{1}{\pi} (2\pi - 0)}$$


$$= \left( \frac{V_m}{2} \right)$$

H.W.R.  $\Rightarrow V_{rms} = \frac{V_m}{2}$

F.W.R.  $\Rightarrow V_{rms} = \frac{V_m}{\sqrt{2}}$


H.W.

Q.3

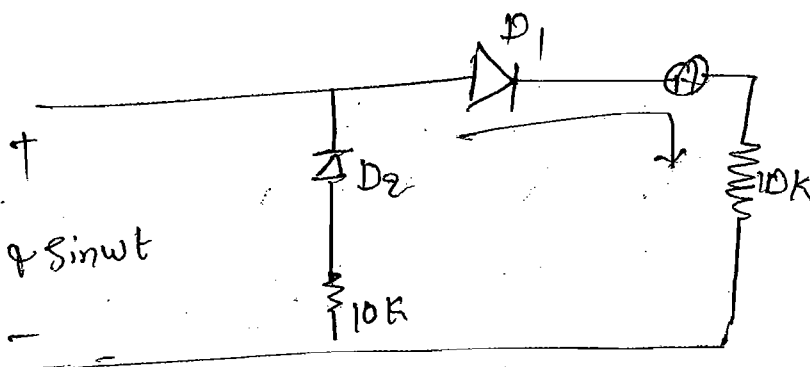

$$V_{ave} = \frac{V_m}{\pi} = \frac{V}{\pi}$$



$$I_{ave} = \frac{V}{\pi \cdot 10}$$

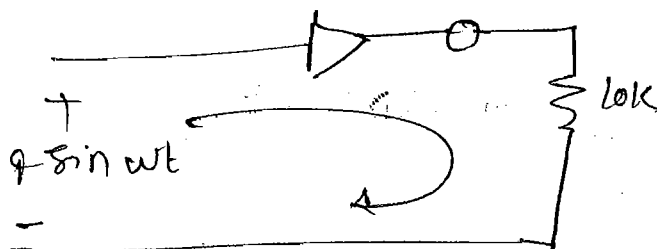

$$I_{ave} = 0.1 \frac{V}{\pi}$$

# \* Full Wave Rectifier :-

(33)

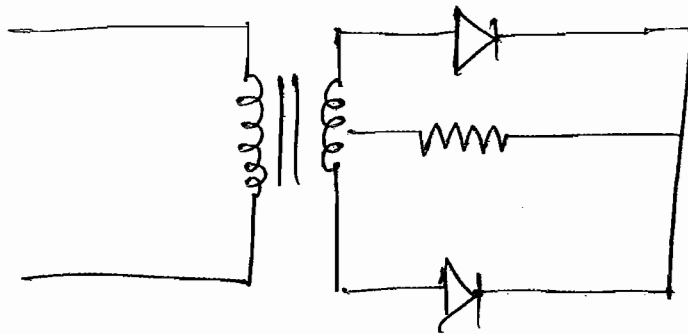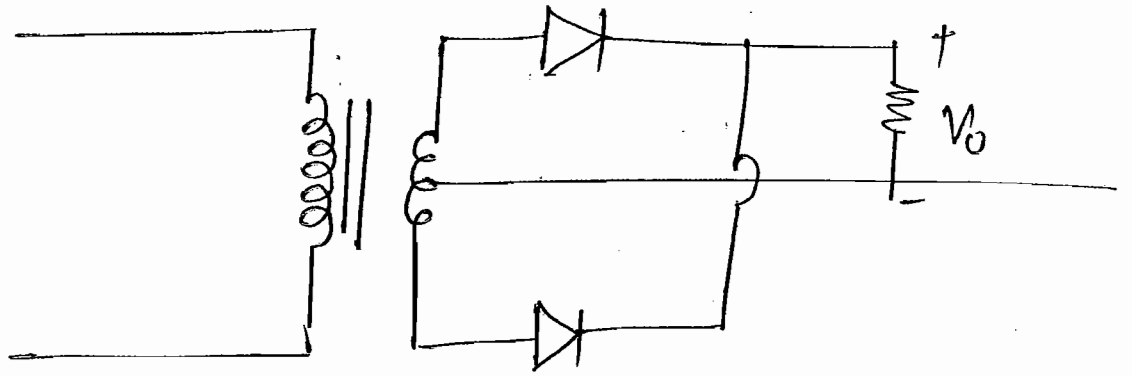

(31)


$$V_m = 10$$



$$V_{ave} = \frac{2V_m}{\pi}$$

$$= \frac{20}{\pi}$$

$$I_{av.} = \frac{V_{ave}}{K} = \frac{20}{\pi} = \frac{20}{\pi} \text{ mA} \quad \underline{10 \text{ mA}}$$

(32)

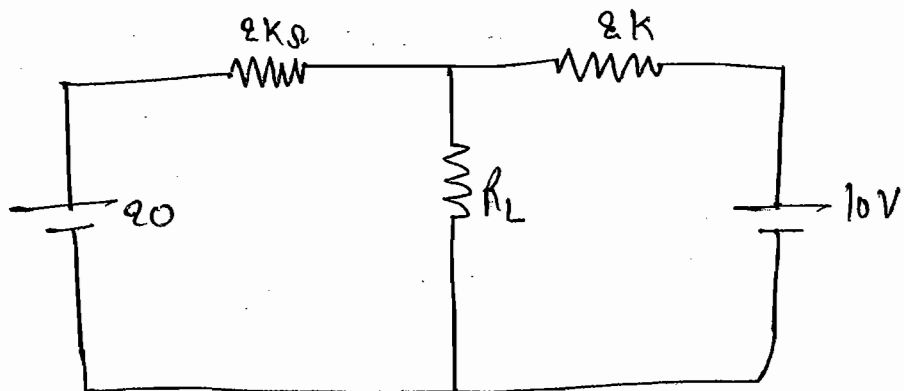

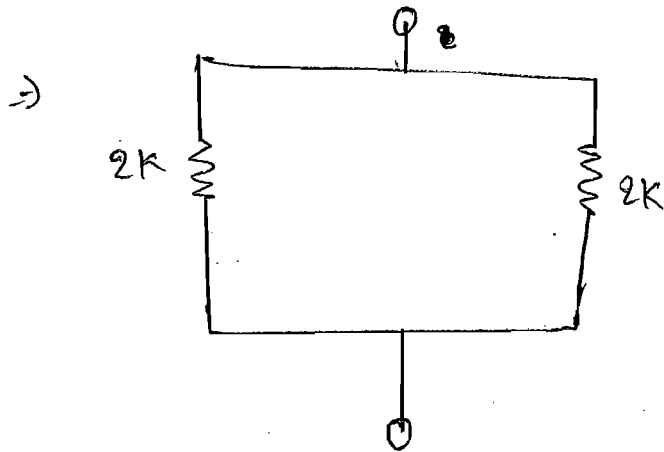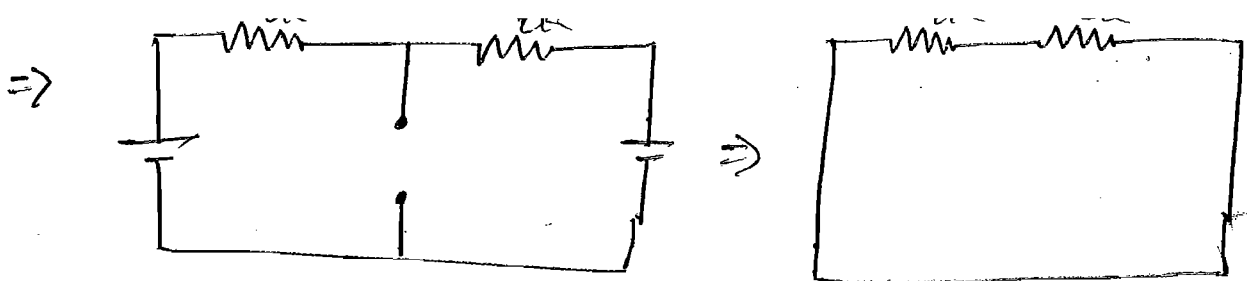


\* Thevenin's Theorem :-



$V_{th} = \text{Open circuit voltage} = V_{oc}$ .

For thevenin's resistance

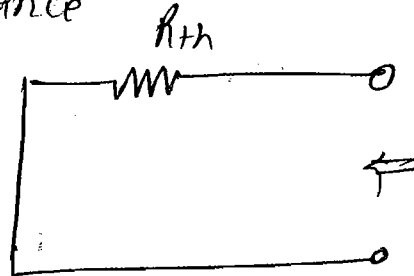


Voltage ~~is~~ 0



$I_{source} = 0$

To calculate thevenin's resistance ~~and~~ short the voltage source and open the current source.

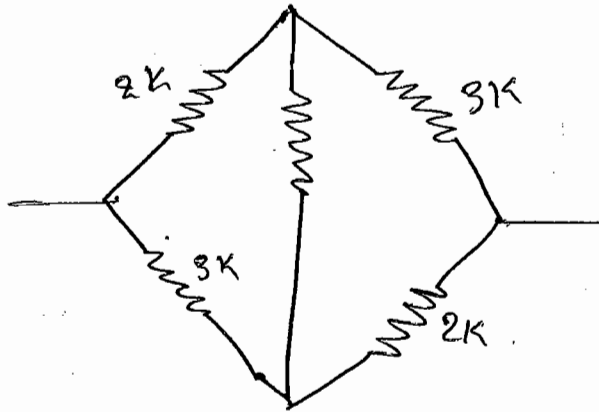Q. For the given circuit diagram calculate thevenin voltage and thevenin's resistance



Sol<sup>n</sup>

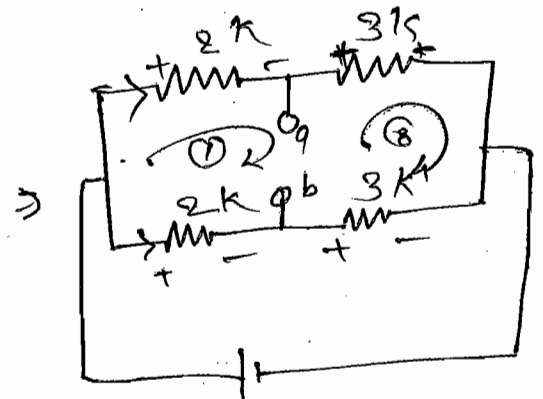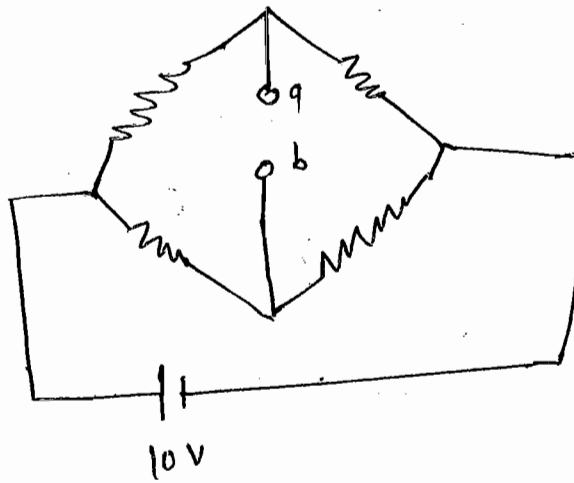

$$I_1 = \frac{V}{R} = \frac{10}{5} = 2 \text{ m.A}$$

$$I_2 = \frac{10}{5} = 2 \text{ m.A}$$

loop-①

$$+I_1 \times 2k + V_{th} - I_2 \cdot 3k = 0$$

$$V_{th} = I_2 \times 3k - I_1 \times 2k$$

$$V_{th} = 2 \times 3 - 2 \times 2$$

$$= 6 - 4$$

$$\boxed{V_{th} = 2 \text{ V}}$$





loop ②

$$-V_{th} + I_1 \cdot 3k - I_2 \cdot 2k = 0$$

$$V_{th} = I_1 \times 3k - I_2 \times 2k$$

$$\boxed{V_{th} = 2 \text{ V}}$$

To calculate thevenin's resistance -

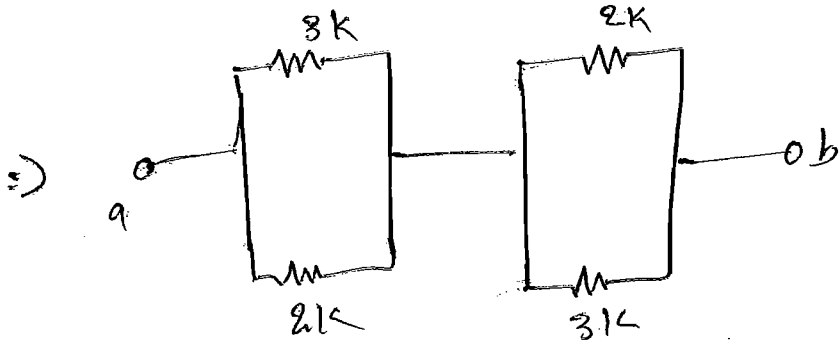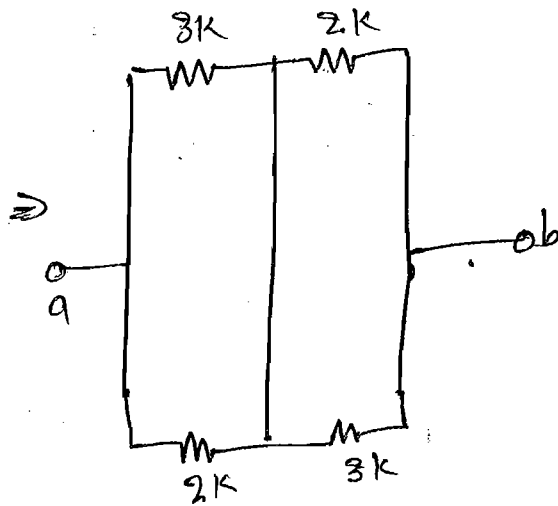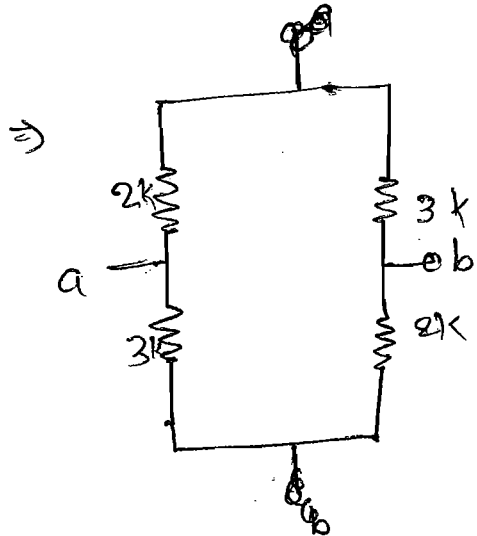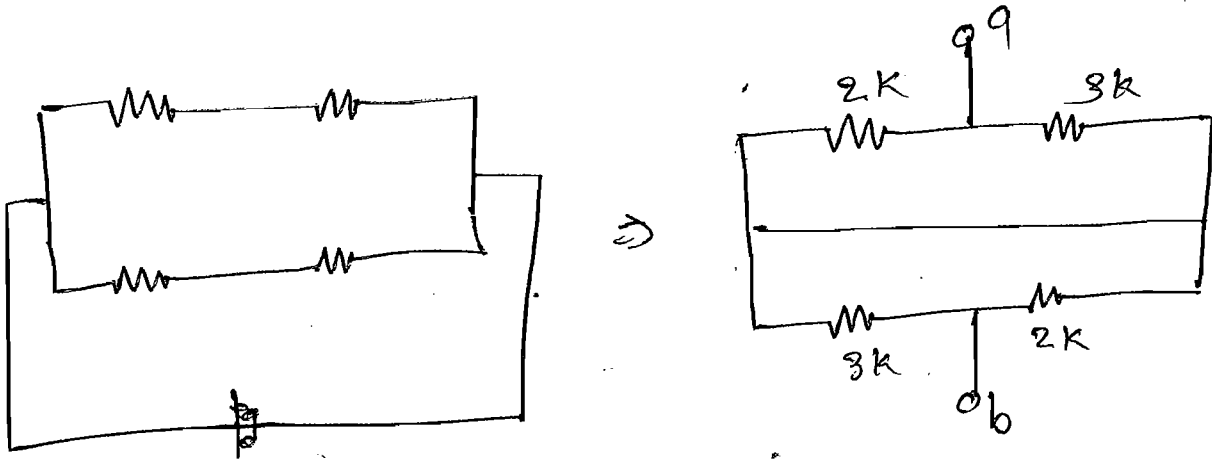


$$\Rightarrow R_{th} = \frac{3 \times 2}{3 + 2} + \frac{3 \times 2}{3 + 2}$$

$$= \frac{6}{5} + \frac{6}{5}$$

$$R_{th} = \frac{12}{5} \Omega$$

Q.32

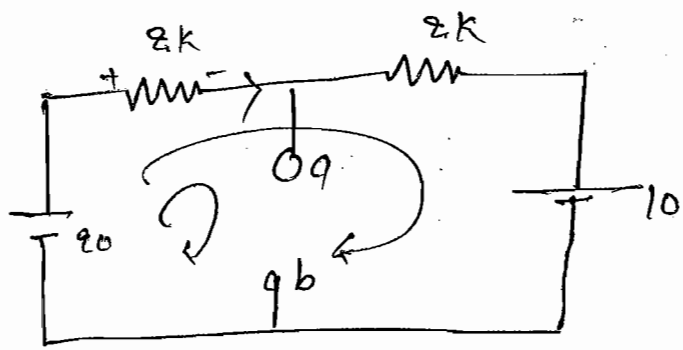

$$-20 + I \times 2k + I \times 2k + 10 = 0$$

$$I \times 4k = 10$$



$$I = 2.5 \text{ m.A}$$

~~$-V_{th} + I \times 2k + 10 = 0$~~   
 ~~$V_{th} = 10 + I \times 2k$~~

$$-V_{th} + I \times 2k + 10 = 0$$

$$V_{th} = 10 + I \times 2k$$


$$10 + 5 = 15 \text{ V}$$

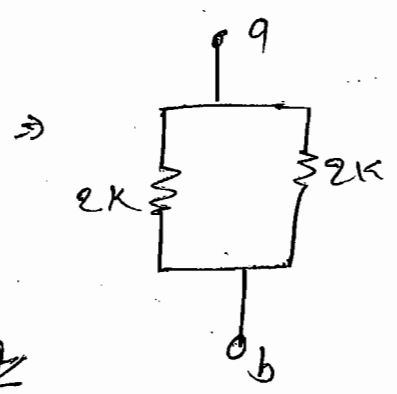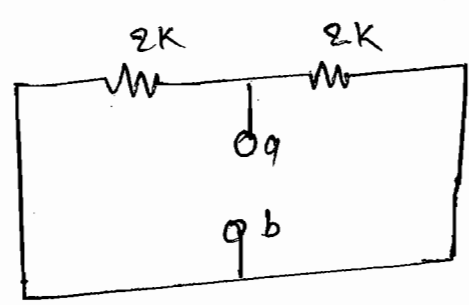


$$R_{th} = \frac{2 \times 2}{2 + 2} = \frac{2}{2}$$

$$R_{th} = 1 \Omega$$

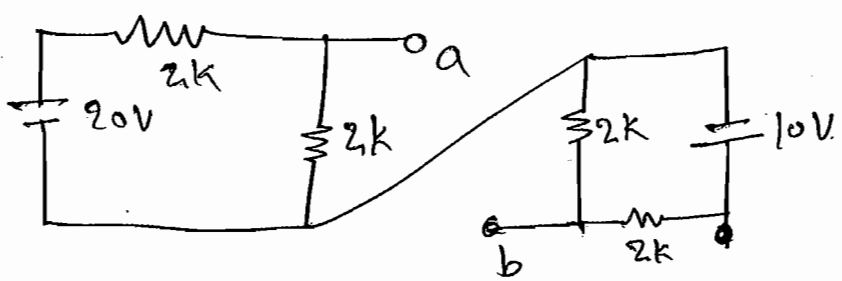Q. For the given circuit diagram calculate Thven's Voltage and Thven's resistance.



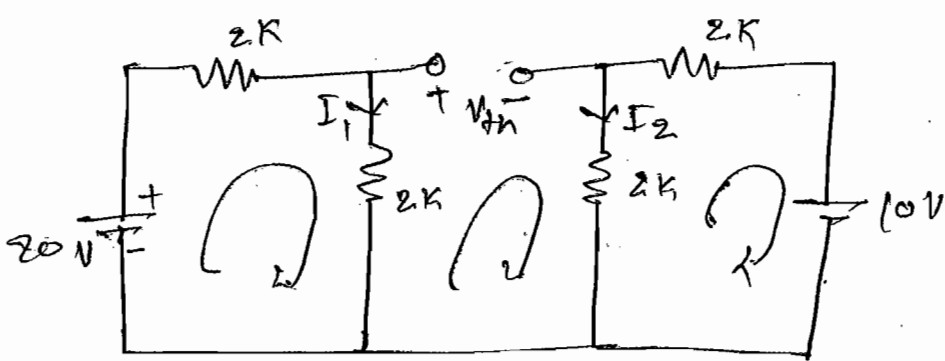

$$-10 + I_2 \cdot 2k + I_2 \cdot 2k = 0$$

$$I_2 = \frac{10}{4k} = 2.5 \text{ mA}$$

$$-20 + I_1 \cdot 2k + I_1 \cdot 2k = 0$$

$$I_1 = \frac{20}{4k} = 5 \text{ mA}$$

$$V_{th} + I_2 \cdot 2k - 2k \times I_1 = 0$$


$$V_{th} = 2k \times I_1 - I_2 \times 2k$$

$$= 2k \times 5 - \cancel{2k \times 2.5} \quad 2.5 \times 2$$

$$= 10 - 5$$

$$\boxed{V_{th} = 5V}$$

for  $R_{TH}$

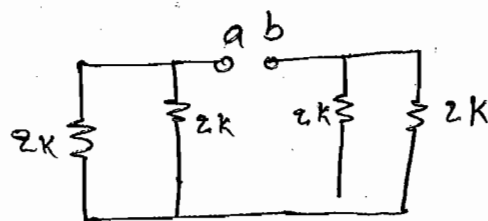


a

$$\boxed{R_{TH} = 2k}$$




69) find  $v$  b/w  $a$  &  $b$ .

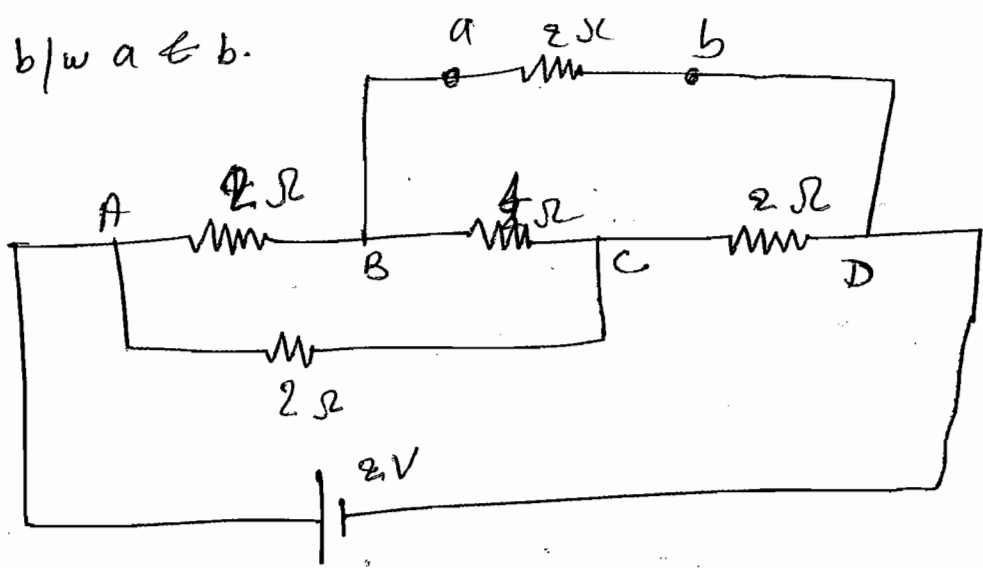


sol<sup>n</sup>

$$\frac{2k}{2k} = \frac{2k}{2k}$$

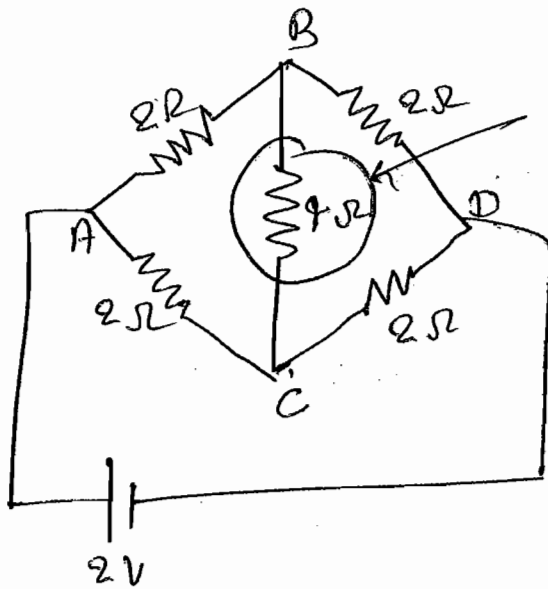


Replace.

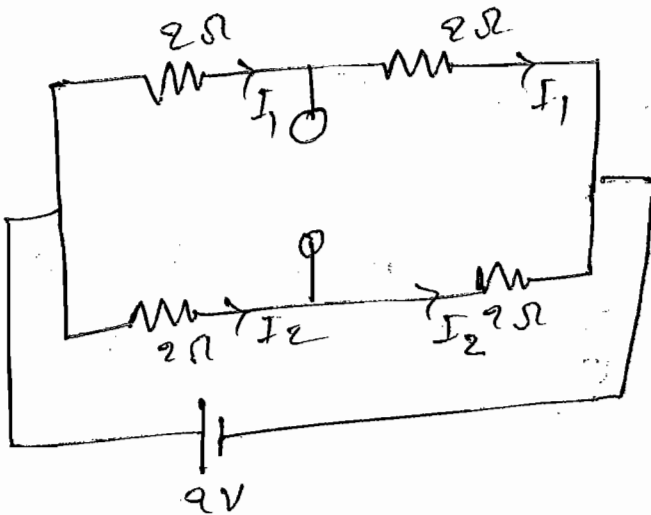ideal  
It is a wheatstone  
bridge. So current  
flow through galvanometer  
is 0 so no  
current flow through  
 $4\Omega$  so we remove  
it.



$\Rightarrow$

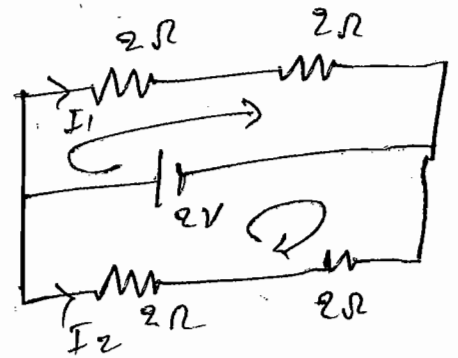


$$-2 + I_1 \cdot 2 + I_1 \cdot 2 = 0$$

$$I_1 = \frac{2}{4} = 0.5 \text{ mA}$$

$$\text{So } I_2 = 0.5 \text{ mA}$$

37

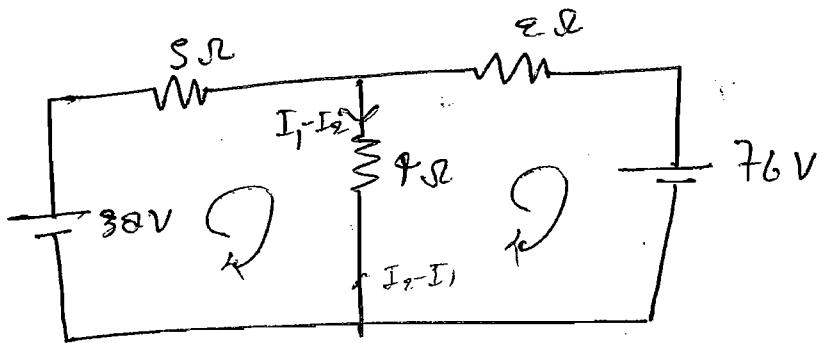

$$-38 + I_1 \times 5 + (I_1 - I_2) \times 9 = 0$$

$$9I_1 - 9I_2 = 38 \quad \text{--- (1) } \times 6$$

$$+76 + 2I_2 + 9(I_2 - I_1) = 0$$

$$-9I_1 + 11I_2 = -76$$

$$9I_1 - 6I_2 = 76 \quad \text{--- (2) } \times 9$$

$$54I_1 - 24I_2 = 38 \times 6$$

$$16I_1 - 9I_2 = 76 \times 9 = 684$$


$$-28I_1 = 38 \times 6 - 76 \times 9$$

$$I_1 = 2$$

$$I_2 = -16$$

Hence  $9 \times 2 - 9 \times (-16) = 180$

$$I_2 = 16$$

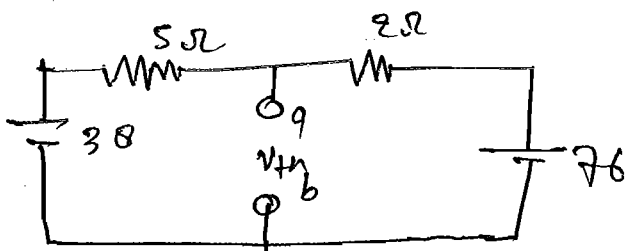

$$-38 + 5I_1 + 2I_1 + 76 = 0$$

$$I_1 = \frac{-38}{7}$$

$$-30 + 5I_1 + V_{th} = 0$$

$$V_{th} = -5I_1 + 30$$

$$= -5 \times \frac{-35}{7} - 30$$

$$= \frac{5 \times 30 + 7 \times 30}{7}$$

$$V_{th} = 6.5 \text{ V.}$$

$$-V_{th} + 2I_1 + 76 = 0$$




$$-V_{th} = -76 - 2I_1$$

$$V_{th} = 76 + 2 \times \left( \frac{-30}{7} \right)$$

$$V_{th} = 76 - \frac{60}{7}$$

$$V_{th} = 6.5 \text{ V}$$


Q.34

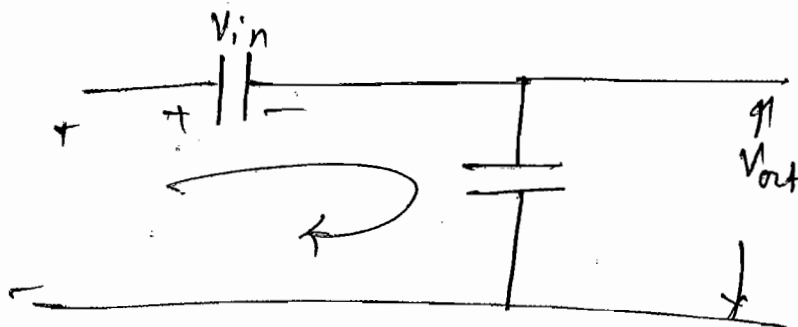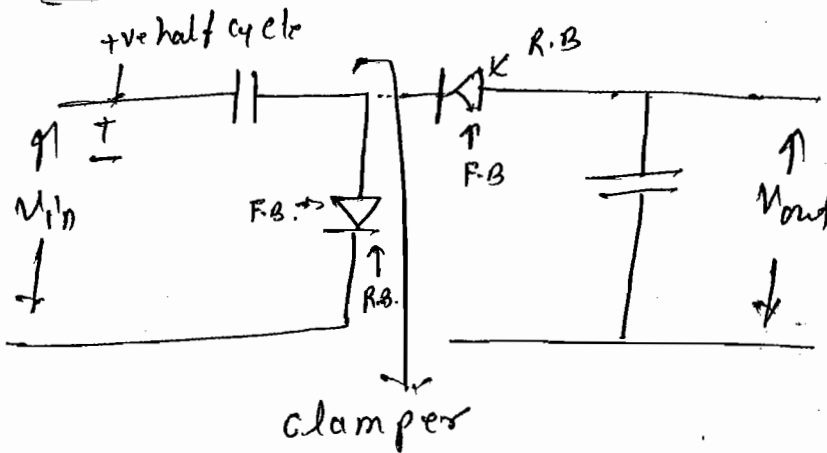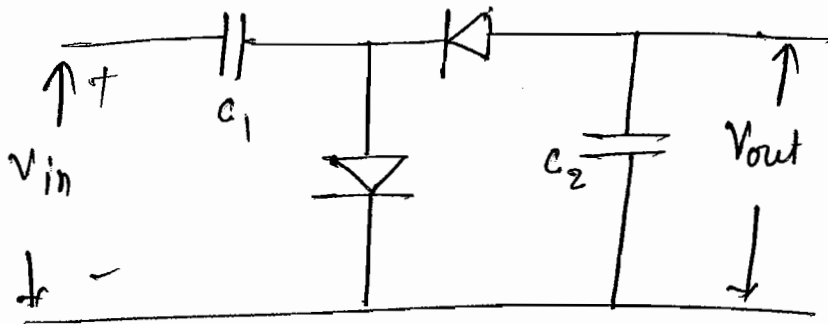

$$+V_{in} + V_{in} - V_{out} = 0$$

$$V_{out} = 2V_{in}$$

(11)

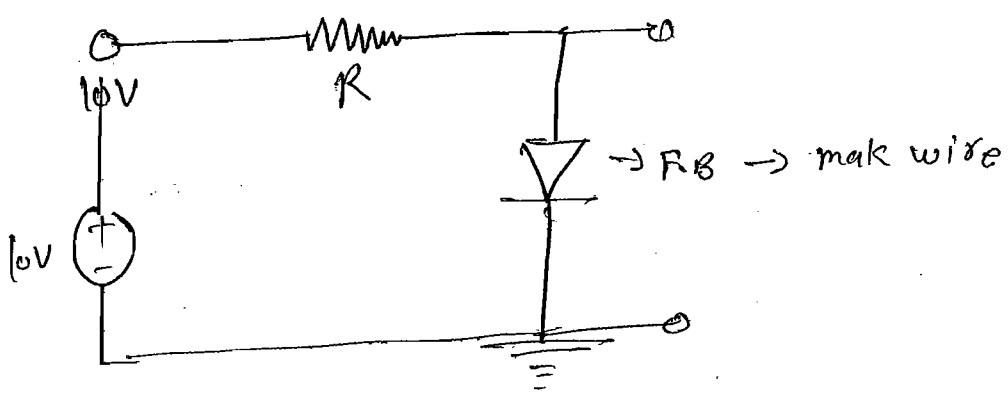


$$-10 + IR = 0$$

$$R = \frac{10}{I}$$


$$R = \frac{10}{10} = 1$$

$$R = 1 \text{ k}\Omega$$


Q.7D

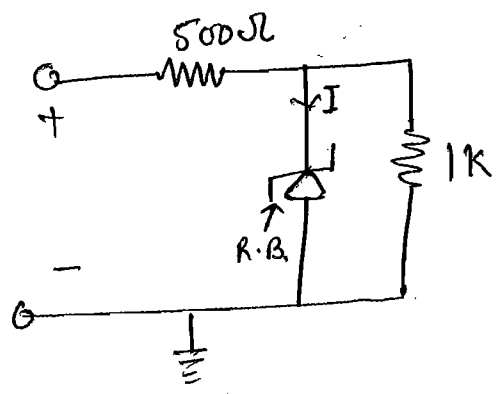



When Zener is R.B.  
then -

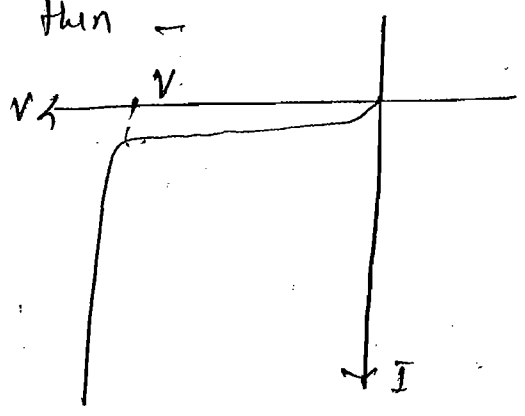



(a)

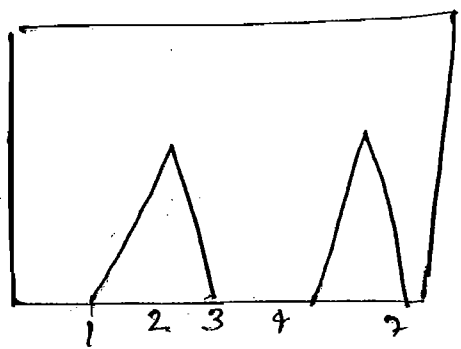

39

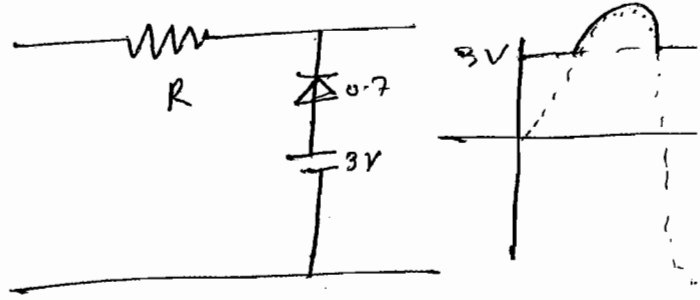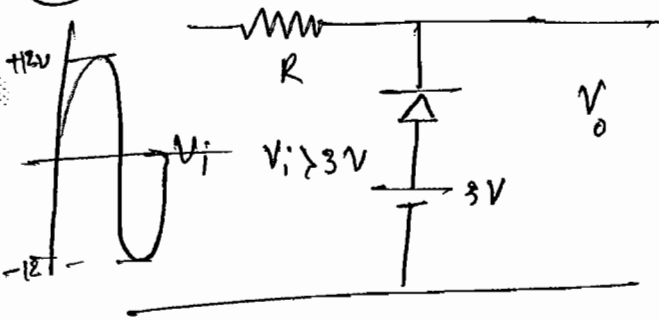

⇒

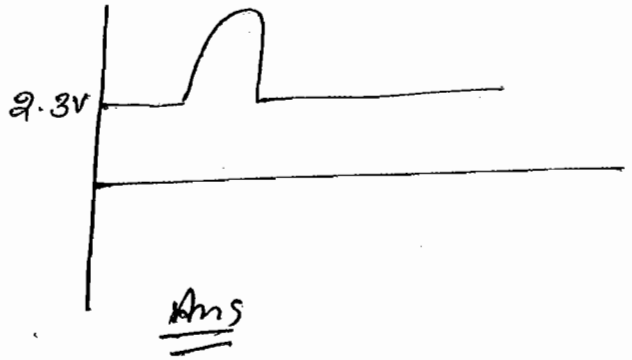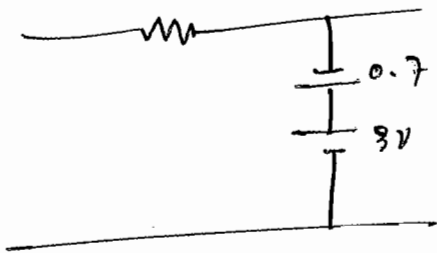

Ans

95

$$\frac{O/P}{I/P} = \text{gain}$$


$$20 \log \left( \frac{O/P}{I/P} \right) = -50 \text{ dB}$$

$$\log \left( \frac{O/P}{I/P} \right) = \frac{-50}{20} = -2.5$$


$$O/P = I/P \times 10^{-2.5}$$

=

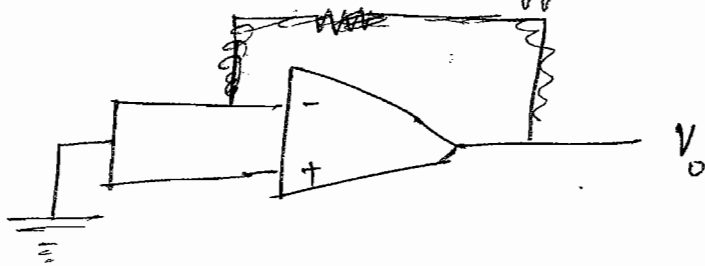When no input is applied some output voltage is achieved called output offset voltage ( $V_{oo}$ ).



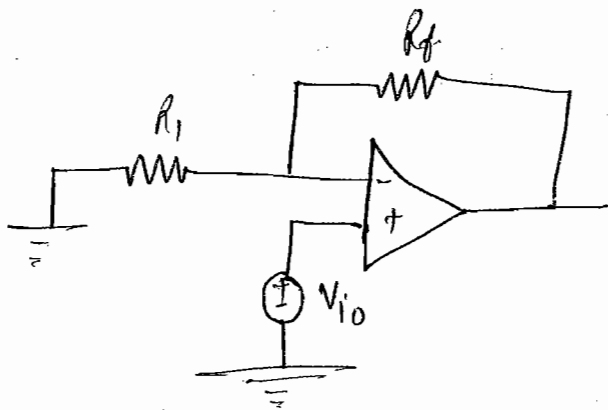To cancel the output offset voltage some input is applied in non-inverting terminal is called as input offset voltage ( $V_{io}$ ).



$$\frac{V_{oo}}{i_o} = \left(1 + \frac{R_f}{R_1}\right)$$

$$V_{oo} = +V_{io} \left(1 + \frac{R_f}{R_1}\right)$$

\* CMRR (Common mode Rejection Ratio) :-

$$\frac{V_o}{V_i} = A = \frac{V_o}{V_d}$$

$$V_o = A_d V_d$$


$A_d$  = differential gain

$V_d$  = differential input voltage

Ex -

due to  
closer  
two signals  
produces  
interference  
pattern. So

difference of the input inters.

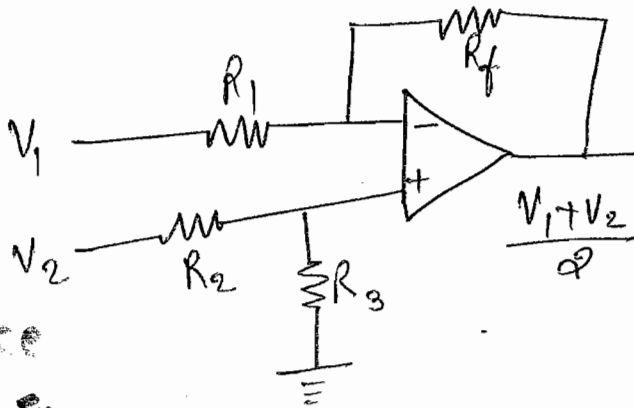

The ideal value of CMRR is must be  $\infty$ .

$$V_o = A_d V_d + A_c V_c \quad \frac{V_1 + V_2}{2}$$

$$CMRR = \frac{A_d}{A_c} = \infty$$

Q. for the given output voltage relation calculate CMRR.


Sol<sup>n</sup>

$$V_o = 10 (V_2 - V_1) \neq 0$$

$$V_o = A_d V_d + A_c V_c$$

$$CMRR = \frac{A_d}{A_c} = \frac{10}{0} = \infty \quad R$$

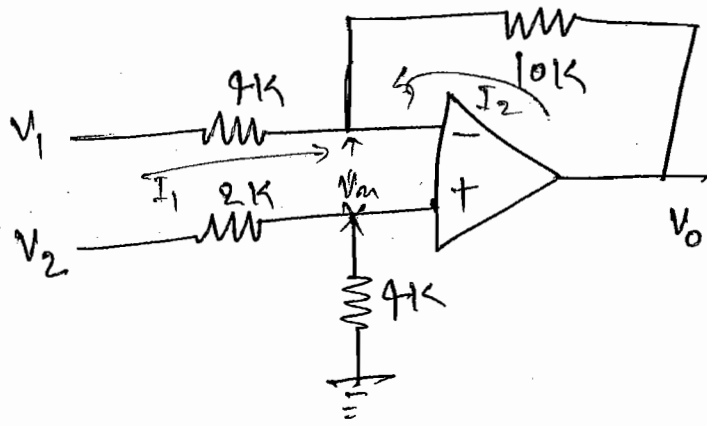Q1 For the given circuit diagram calculate EMRR.



$$V_o = A_d V_d + A_c V_c$$

$$V_{in} = \frac{V_2 R_2}{R_1 + R_2} = \frac{V_2 \times 4K}{4 + 2} = \frac{4V_2}{6} = \frac{2}{3} V_2$$

$$i_1 + i_2 = 0$$

$$\frac{V_1 - V_{in}}{4K} + \frac{V_o - V_{in}}{\frac{10K}{2.5}} = 0$$

$$\frac{V_o - V_{in}}{2.5} = (V_1 - V_{in}) = V_{in} - V_1$$

$$V_o - V_{in} = 2.5 V_{in} - 2.5 V_1$$

$$V_o = 3.5 V_{in} - 2.5 V_1$$

$$V_o = 3.5 \times \frac{2V_2}{3} - 2.5 V_1$$

$$V_o = \frac{7}{3} V_2 - \frac{5}{2} V_1$$

$$V_c = \frac{V_2 + V_1}{2} \Rightarrow 2V_c = V_1 + V_2 \quad \text{--- (I)}$$

$$V_d = \frac{V_2 - V_1}{2} \Rightarrow V_d = V_2 - V_1 \quad \text{--- (II)}$$

$$\Rightarrow \left[ V_2 = V_c + \frac{V_d}{2} \right] \text{--- (III)} \quad 2V_c + V_d = 2V_2$$



$$(i) - (ii)$$

$$2V_c = V_1 + V_2$$

$$V_d = V_2 - V_1$$

$$2V_c - V_d = 2V_1$$

$$\boxed{V_1 = V_c - \frac{V_d}{2}} \quad (iv)$$

$$V_o = \frac{7}{3} V_2 - \frac{5}{2} V_1$$

$$V_o = \frac{7}{3} \left( V_c + \frac{V_d}{2} \right) - \frac{5}{2} \left( V_c - \frac{V_d}{2} \right)$$

~~$$V_o = V_c \left( \frac{7}{3} \right)$$~~

$$V_o = \left( \frac{7}{6} V_d - \frac{5}{4} V_d \right) + \left( \frac{7}{3} V_c - \frac{5}{2} V_c \right)$$

$$V_o = V_d \left( \frac{7}{6} + \frac{5}{4} \right) + V_c \left( \frac{7}{3} - \frac{5}{2} \right)$$


$$V_o = V_d \left( \frac{29}{12} \right) + V_c \left( -\frac{1}{6} \right)$$

$$CMRR = \frac{A_d}{A_c} = \frac{\frac{29}{12}}{-\frac{1}{6}} = \frac{-29}{2} \text{ A}$$

$$= -14.5$$

$$= \boxed{14.5}$$

Q. Determine CMRR of given circuit -

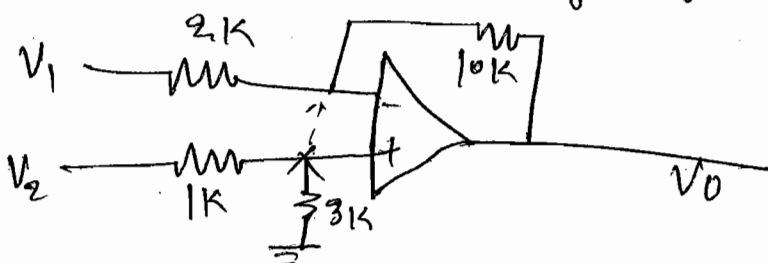

$$V_{a1} = \frac{V_2 \times 3k}{3k + 1k} = \frac{3V_2}{4}$$

$$\frac{V_0 - V_{a1}}{10k} + \frac{V_1 - V_{a1}}{2k} = 0$$

$$\frac{V_0 - \frac{3V_2}{4}}{\frac{10k}{5}} + \frac{V_1 - \frac{3V_2}{4}}{2k} = 0$$

$$V_0 = -5V_1 + \frac{15V_2}{4} + \frac{3V_2}{4}$$

$$V_0 = -5V_1 + \frac{9}{2}V_2$$

$$V_c = \frac{V_1 + V_2}{2}, V_d = V_2 - V_1$$

$$V_1 = V_c - \frac{V_d}{2}$$

$$V_2 = V_c + \frac{V_d}{2}$$

$$V_0 = -5 \left( V_c - \frac{V_d}{2} \right) + \frac{9}{2} \left( V_c + \frac{V_d}{2} \right)$$

$$V_0 = (-5V_c + 2.5V_c) + \left( \frac{5}{2}V_d + \frac{9}{4}V_d \right)$$

$$V_0 = -0.5V_c + \frac{19}{4}V_d$$

$$CMRR = \frac{A_d}{A_c} = \frac{19/4}{-1/2} = \frac{19}{2}$$

Q.39

Sol<sup>n</sup>

$$A_d = 20000$$

$$\text{CMRR} = 80 \text{ dB}$$

$$\text{CMRR} = \left| \frac{A_d}{A_c} \right|$$

$$\text{CMRR} = 20 \log \left| \frac{A_d}{A_c} \right| = 80$$

$$\Rightarrow \log \frac{A_d}{A_c} = 4$$

$$\Rightarrow \frac{A_d}{A_c} = 10^4$$

$$\Rightarrow 20000 = 10^4 A_c$$

$$A_c = \frac{20000}{10000}$$

$$\boxed{A_c = 2}$$

Q.42

Sol<sup>n</sup>

$$\text{gain} = \frac{V_o}{V_{in}} = \frac{1500}{15} = 100$$

$$20 \log 100 = \boxed{40}$$

Power

$$\left. \begin{aligned} \text{Actual gain} &= \frac{P_o}{P_{in}} \\ A_{dB} &= 10 \log \frac{P_o}{P_{in}} \\ &= 10 \log \frac{V_o^2}{R} \cdot \frac{R}{V_{in}^2} = 20 \log \left( \frac{V_o}{V_{in}} \right) \end{aligned} \right\}$$


$$A = \frac{P_o}{P_{in}} = \frac{1500}{1.5} = 1000$$

$$A_{dB} = 10 \log 1000$$

$$= \underline{\underline{30}} \text{ dB}$$

Q. 16

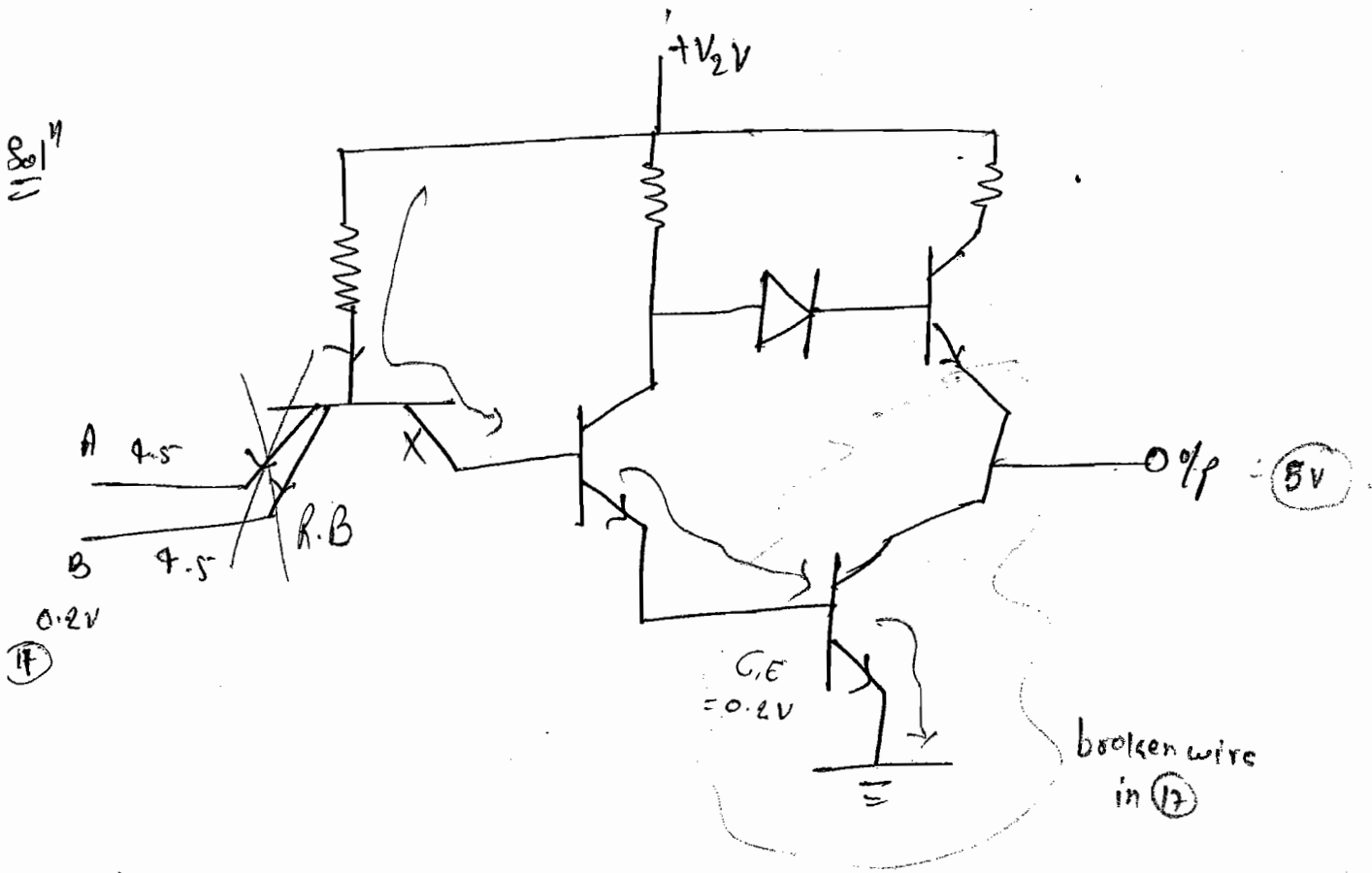
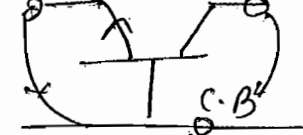
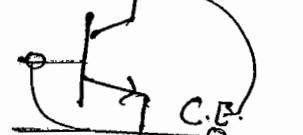
118/11



Ans = 0.2 V.

~~17~~


5V

	C.C. 	C.B. 	C.E. 
$A_I$	$\frac{I_E}{I_B} > 1$	$\frac{I_C}{I_E} \approx 1$	$A > 1$
$A_V$	$A_V = \frac{V_{EC}}{V_{BC}} \approx 1$	$A_V = \frac{V_{CB}}{V_{EB}} > 1$	$A_V = \frac{V_{CE}}{V_{BE}} > 1$
$R_{in}$	high	low	medium
$R_o$	low	high	medium.

$$V_{CE} - V_{BE} - V_{CB} = 0$$

$$V_{CE} = V_{CB} + V_{BE}$$

$$V_{CE} \approx V_{CB}$$

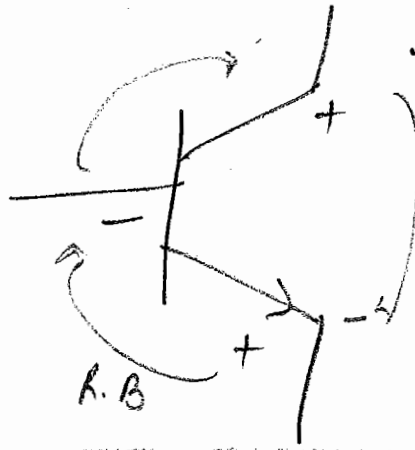

Crate.

~~Q2~~  
half wave  
Rectifier

$$\gamma = \sqrt{\frac{I_{rms}^2}{I_{dc}^2} - 1}$$

$$\gamma = \sqrt{\left(\frac{\frac{I_m}{2}}{\frac{I_m}{\pi}}\right)^2 - 1}$$

$$\gamma = \sqrt{\frac{A^2}{\pi^2} - 1}$$

$$\boxed{\gamma = 1.2} \quad A$$

# Full wave Rectifier

$$\gamma = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$


$$= \sqrt{\frac{\left(\frac{I_m}{\sqrt{2}}\right)^2}{\left(\frac{2I_m}{\pi}\right)^2} - 1}$$

$$= \sqrt{\frac{\frac{1}{2}}{\frac{4}{\pi^2}} - 1}$$

$$= \sqrt{\frac{\pi^2}{8} - 1}$$

$$= 0.46$$


43

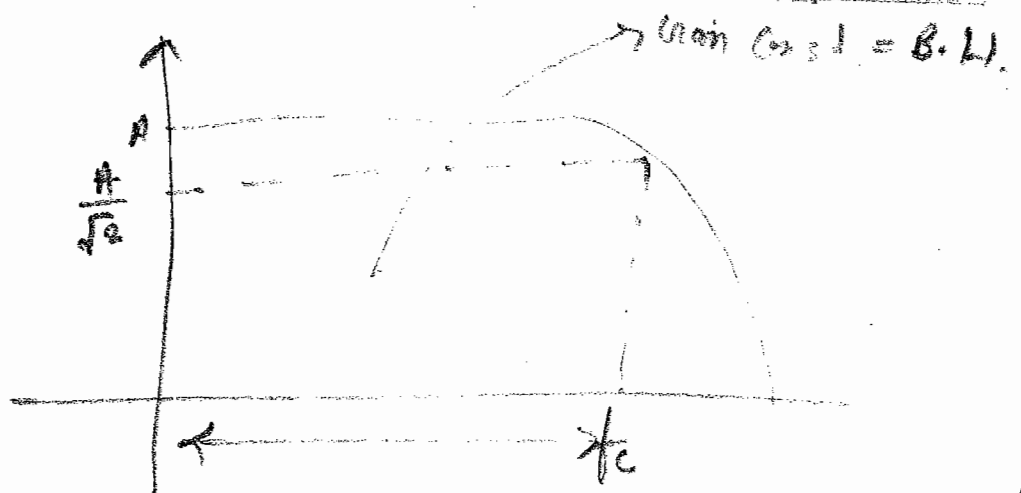


Those group of frequencies where gain is approximately constant is called as B.L.

B.W = upper cut of freq. =  $f_c - 0 = f_c$   
 - lower cut of freq.

High pass filter :-

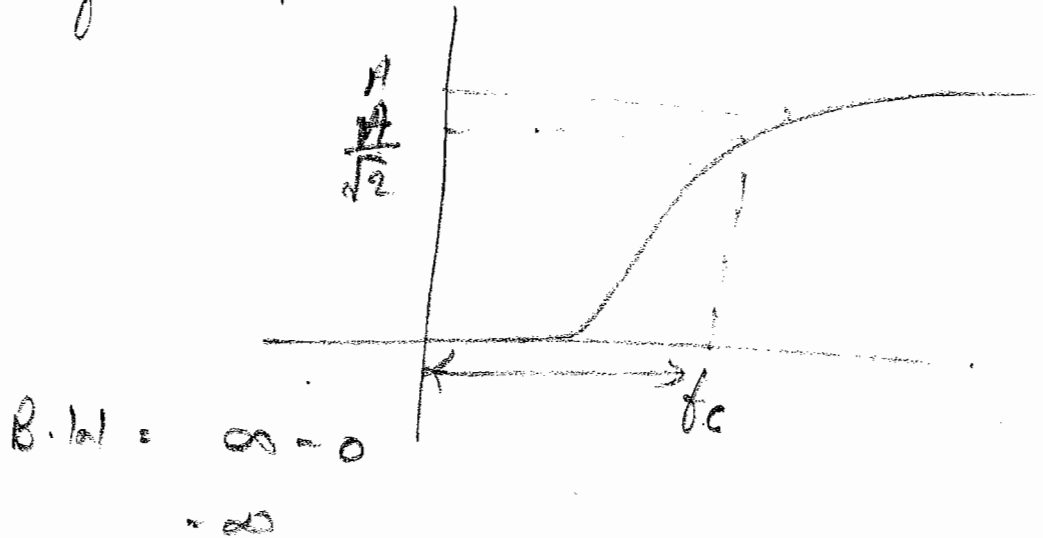


Band Pass

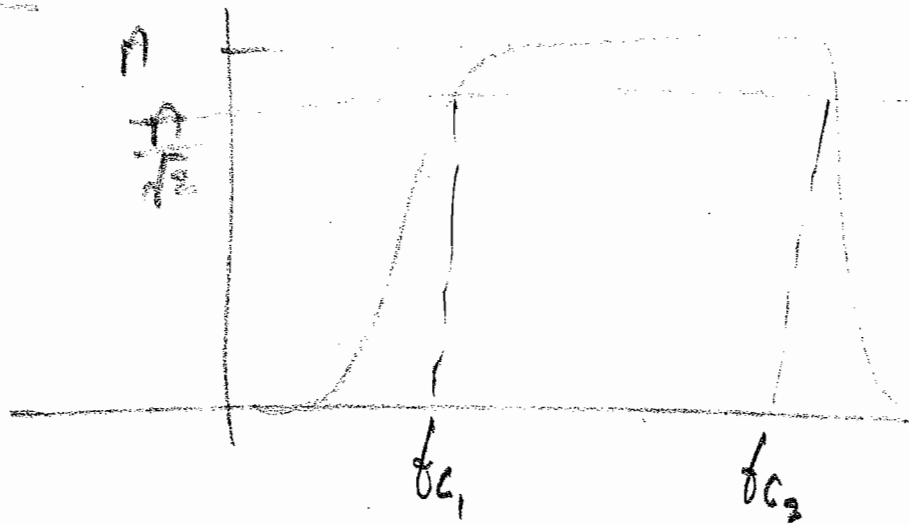


B.W =  $f_{c2} - f_{c1}$

Band Rejected filter

$B.W = \infty - 0$   
 B.W =  $\infty$

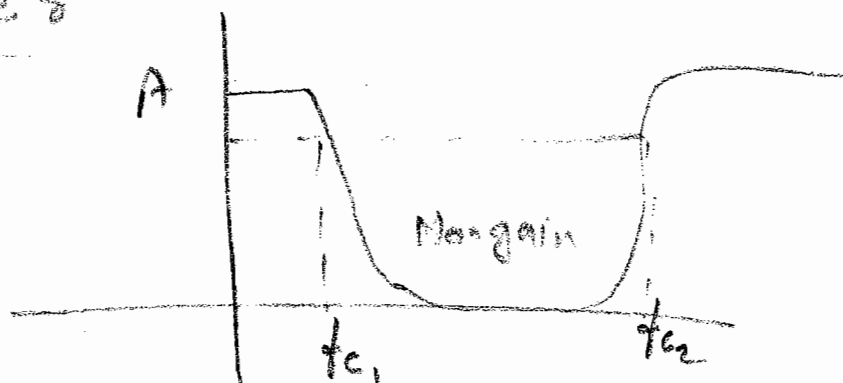

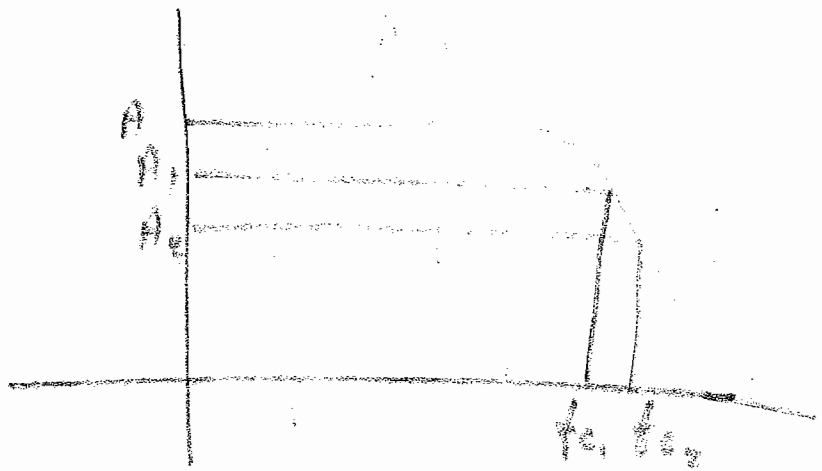Gain  $\times$  Bandwidth product always constant



$$A_1 \times f_{c1} = \text{const}$$

$$A_2 \times f_{c2} = \text{const}$$

$\uparrow$   $f_{c1}$   
 $\downarrow$   $f_{c2}$

Q. 9 (c)

Q. 10

$A = 100$ , feedback = 9.9%


$$\beta = \frac{9.9}{100} = \underline{\underline{0.099}}, \quad f_c = 20 \text{ kHz}$$

$$f_H = 200 \text{ kHz}$$

$$\text{Gain} = \frac{A}{1 + A\beta}$$

$$= \frac{100}{1 + 100 \times 0.099} = \frac{1000}{100} = 10$$

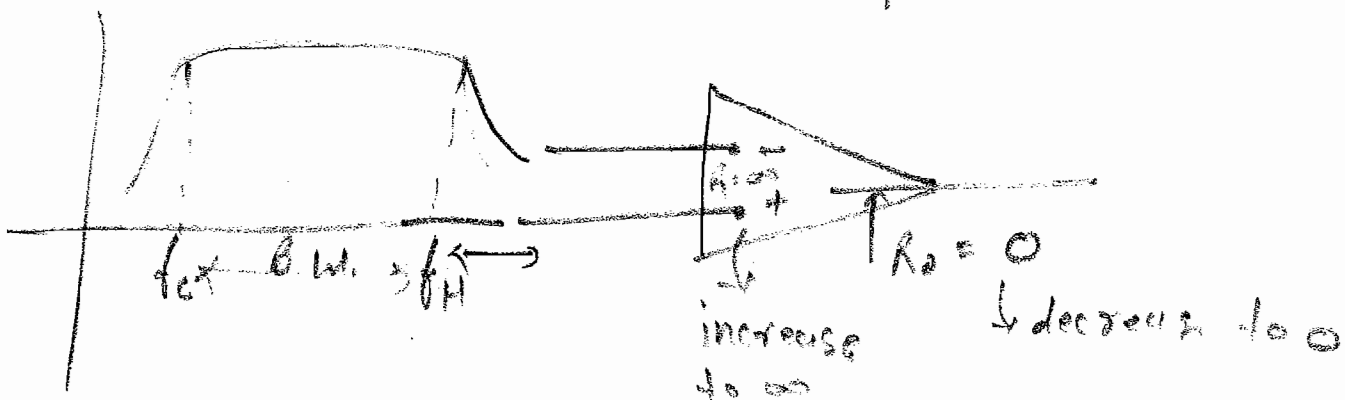$\therefore$  Gain is decrease by 100 times.






$$\begin{aligned} \text{Gain} &= \beta_H * (1 + A\beta) \\ &= 100 * (1 + 1000 * 0.009) \\ &= 100 * (1 + 9) \end{aligned}$$

$$= 1000 \quad \underline{\underline{\Delta}}$$

97


$$\beta = 0.1$$
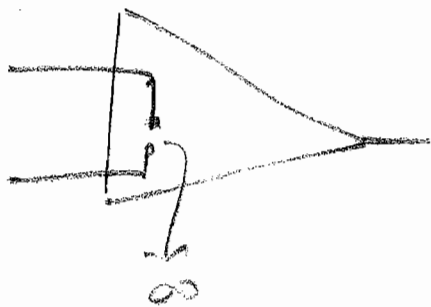
$$A_{CL} = \frac{A}{1 + A\beta} = \frac{500}{1 + 50} = \frac{500}{51} \quad (9.8)$$




$$\begin{aligned} \text{Gain} &= R_{in} * (1 + A\beta) \\ &= 700 \text{ K} * (51) \\ &= 35700 \text{ K} \end{aligned}$$

78

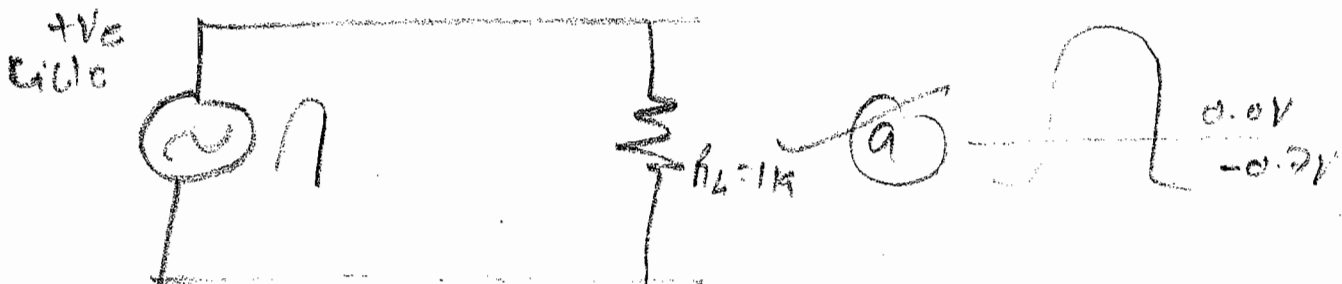

79 Second method.

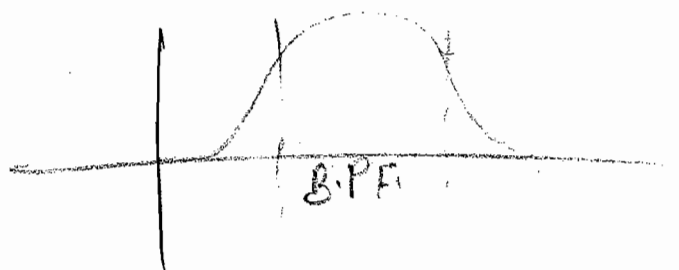

For any LC circuit cut-off freq. at given  
by resonance freq.

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$\omega = \frac{1}{\sqrt{LC}}$$