

LCR Parallel Resonance

Expression for Resonant Frequency:

Parallel resonance circuit is shown in fig(1). One branch of the resonant circuit consists resistance R in series with an inductance L. Capacitor C is connected parallel to the RL combination in other branch. An AC source is applied across this parallel combination.

The admittance of the circuit is given by

$$y = \frac{1}{z} = \frac{1}{R + j\omega L} + \frac{1}{\frac{1}{j\omega C}}$$

$$y = \frac{1}{z} = \frac{1}{R + j\omega L} + j\omega C$$

or
$$\frac{1}{z} = \frac{1}{R + j\omega L} \times \frac{(R - j\omega L)}{(R - j\omega L)} + j\omega C$$

or
$$\frac{1}{z} = \frac{(R - j\omega L)}{(R^2 - j^2\omega^2 L^2)} + j\omega C$$

or
$$\frac{1}{z} = \frac{(R - j\omega L)}{(R^2 + \omega^2 L^2)} + j\omega C \quad (\because j^2 = -1)$$

or
$$\frac{1}{z} = \frac{R}{(R^2 + \omega^2 L^2)} - \frac{j\omega L}{(R^2 + \omega^2 L^2)} + j\omega C$$

or
$$\frac{1}{z} = \frac{R}{(R^2 + \omega^2 L^2)} - j\omega \left[\frac{L}{(R^2 + \omega^2 L^2)} - C \right] \quad \text{----- (1)}$$

At resonance the reactance part of Eqn(1) is equal to zero

$$\therefore \left[\frac{L}{(R^2 + \omega^2 L^2)} - C \right] = 0$$

or
$$\frac{L}{(R^2 + \omega^2 L^2)} = C$$

or
$$L = C(R^2 + \omega^2 L^2)$$

or
$$(R^2 + \omega^2 L^2) = \frac{L}{C} \quad \text{----- (2)}$$

or
$$\omega^2 L^2 = \frac{L}{C} - R^2$$

or
$$\omega_0^2 = \frac{L}{CL^2} - \frac{R^2}{L^2}$$

or
$$\omega_0^2 = \frac{1}{LC} - \frac{R^2}{L^2}$$

or
$$\omega_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}}$$

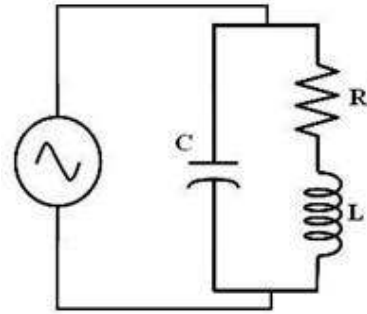


Fig (1)

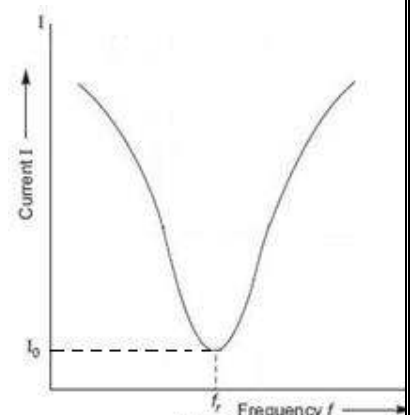


Fig (2)

or
$$2\pi f_0 = \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad (\because \omega_0 = 2\pi f_0)$$

or
$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{R^2}{L^2}} \quad \text{----- (3)}$$

where f_0 = resonant frequency of LCR parallel circuit

Dynamic Resistance

The resistance at resonance is known as dynamic resistance. Consider the following equation.

$$\frac{1}{Z} = \frac{R}{(R^2 + \omega^2 L^2)} - j\omega \left[\frac{L}{(R^2 + \omega^2 L^2)} - C \right]$$

at resonance
$$\left[\frac{L}{(R^2 + \omega^2 L^2)} - C \right] = 0$$

$$\therefore \frac{1}{Z} = \frac{R}{(R^2 + \omega^2 L^2)} \quad \text{----- (1)}$$

we know that $(R^2 + \omega^2 L^2) = \frac{L}{C}$, substituting in Eqn(1), we get

$$\frac{1}{Z} = \frac{R}{L/C}$$

Or
$$\frac{1}{Z} = \frac{RC}{L}$$

or
$$Z_0 = r_d = \frac{L}{RC} \quad \text{----- (2)}$$


where r_d is known as dynamic resistance.

Bandwidth

Bandwidth is defined as the band of frequencies between two points on either side of resonant frequency where impedance falls to $\frac{1}{\sqrt{2}}$ times of value at resonance.

Impedance of the LCR parallel circuit is given by
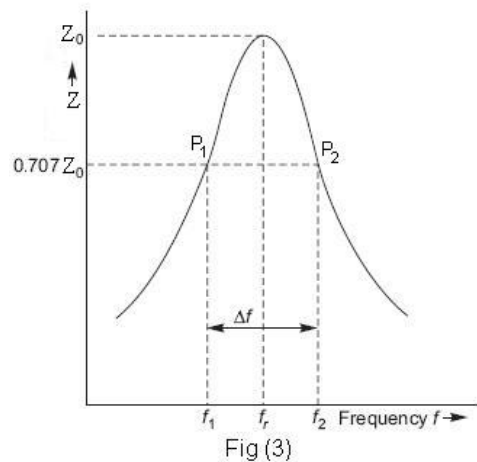
$$Z = \frac{(R + j\omega L) \frac{1}{j\omega C}}{\left(R + j\omega L + \frac{1}{j\omega C} \right)}$$



or
$$Z = \frac{(R + j\omega L)}{j\omega C \left(R + j\omega L + \frac{1}{j\omega C} \right)}$$

or
$$Z = \frac{(R + j\omega L)}{(j\omega RC - \omega^2 LC + 1)}$$

where $R \ll \omega L$ then R can be neglected from the above equation.

$$Z = \frac{j\omega L}{j\omega RC + (1 - \omega^2 LC)}$$

Taking modulus on both sides of the above equation, we get

$$|Z| = \frac{\omega L}{\sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}} \quad \text{----- (1)}$$

Multiplying numerator and denominator of eqn (1) with $\frac{1}{\omega RC}$, we get

$$|Z| = \frac{\omega L \times \frac{1}{\omega RC}}{\frac{1}{\omega RC} \sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}}$$

or
$$|Z| = \frac{\frac{L}{RC}}{\frac{1}{\omega RC} \sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}}$$

or
$$|Z| = \frac{Z_0}{\frac{1}{\omega RC} \sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}} \quad \left(\because Z_0 = \frac{L}{RC} \right)$$

or
$$|Z| = \frac{Z_0 \omega RC}{\sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}}$$

but $|Z| = \frac{Z_0}{\sqrt{2}}$

$$\therefore \frac{Z_0}{\sqrt{2}} = \frac{Z_0 \omega RC}{\sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}}$$

or
$$\frac{1}{\sqrt{2}} = \frac{\omega RC}{\sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2}}$$

or
$$\sqrt{\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2} = \omega RC \sqrt{2} \quad \text{----- (2)}$$

squaring on both sides of eqn(2), we get

$$\omega^2 R^2 C^2 + (1 - \omega^2 LC)^2 = 2\omega^2 R^2 C^2$$

or
$$(1 - \omega^2 LC)^2 = 2\omega^2 R^2 C^2 - \omega^2 R^2 C^2$$

or
$$(1 - \omega^2 LC)^2 = \omega^2 R^2 C^2$$

taking square root on both sides of the above equation, we get

$$1 - \omega^2 LC = \pm \omega RC$$

or
$$\omega^2 LC \pm \omega RC - 1 = 0 \quad \text{----- (3)}$$

Eqn (3) is a quadratic equation in ω and will yield two values. The two values ω_1 and ω_2 and they can be obtained as follows.

$$= \frac{\pm RC \pm \sqrt{R^2 C^2 + 4LC}}{2LC}$$

or
$$= \frac{\pm RC}{2LC} \pm \frac{\sqrt{R^2 C^2 + 4LC}}{2LC}$$

or
$$= \frac{\pm RC}{2LC} \pm \sqrt{\left(\frac{R^2 C^2}{4L^2 C^2} + \frac{4LC}{4L^2 C^2}\right)}$$

or
$$= \frac{\pm R}{2L} \pm \sqrt{\left(\frac{R^2}{4L^2} + \frac{1}{LC}\right)}$$

as $R \ll \omega L$, therefore $\frac{R^2}{4L^2}$ can be ignored from the above equation, we get

$$= \frac{\pm R}{2L} \pm \sqrt{\frac{1}{LC}} \text{ ----- (4)}$$

Let $\frac{R}{2L} = \alpha$, and we know that $\sqrt{\frac{1}{LC}} = \omega_0$, substituting these values in the equ (4) we get

$$= \pm \alpha \pm \omega_0$$

Two roots can be written as follows

$\omega_2 = \omega_0 + \alpha$ and $\omega_1 = \omega_0 - \alpha$ (since angular frequency can not be negative)

Therefore Bandwidth $\therefore \Delta\omega = \omega_2 - \omega_1$

substituting ω_1 and ω_2 values in the above equation, we get

$$\Delta\omega = \omega_0 + \alpha - (\omega_0 - \alpha)$$

or
$$\Delta\omega = \omega_0 + \alpha - \omega_0 + \alpha$$

or
$$\Delta\omega = 2\alpha \text{ ----- (5)}$$

but
$$\alpha = \frac{R}{2L}$$

therefore
$$\Delta\omega = \frac{2R}{2L}$$

or
$$\Delta\omega = \frac{R}{L}$$

or
$$\Delta\omega = \omega_2 - \omega_1 = (2\pi f_2 - 2\pi f_1) = \frac{R}{L}$$

or
$$2\pi(f_2 - f_1) = \frac{R}{L}$$

$$(f_2 - f_1) = \frac{R}{2\pi L}$$

Therefore bandwidth
$$\Delta f = (f_2 - f_1) = \frac{R}{2\pi L} \text{ ----- (6)}$$

Quality Factor (Q – Factor)

When voltage V is applied to the parallel LCR circuit, the current flowing through the circuit at resonance is given by

$$I = \frac{V}{r_d} \quad \text{----- (1)}$$

Where r_d is dynamic resistance = $\frac{L}{RC}$

Substituting r_d value in eqn (1), we get

$$I = \frac{V}{L/RC}$$

or $I = \frac{VRC}{L}$

from above equation $V = \frac{IL}{RC}$ ----- (2)

Voltage across the capacitor = V_C

Voltage across the inductor = V_L

From fig (4) voltage across capacitor (V_C) = voltage across inductor (V_L) = applied voltage (V)
(Since the capacitor and the inductor are parallel to the applied voltage)

Voltage across capacitor $V = I_C \times \frac{1}{\omega_0 C}$

$$I_C = V\omega_0 C \quad \text{----- (3)}$$

Substituting V value from eqn(2) in eqn(3) we get

$$I_C = \frac{IL}{RC} \omega_0 C$$

or $I_C = \frac{IL\omega_0}{R}$

Voltage across the inductor is $V = I_L \times \omega_0 L$

or $I_L = \frac{V}{\omega_0 L}$ ----- (4)

substituting V value from eqn(2) in eqn (4), we get

$$I_L = \frac{IL}{RC} \times \frac{1}{\omega_0 L}$$

or $I_L = \frac{I}{RC\omega_0}$ ----- (5)

The Q-factor is defined as the magnification of the current at resonance

$$Q = \frac{I_C}{I} = \frac{I_L}{I}$$

From eqn(4) we have $\frac{I_C}{I} = \frac{\omega_0 L}{R}$

$\therefore \frac{I_C}{I} = Q = \frac{\omega_0 L}{R}$ ----- (6)

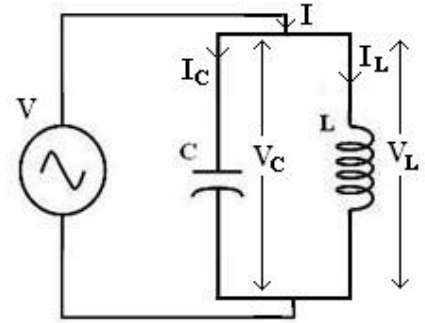


Fig (4)

From eqn (5) we have

$$\frac{I_L}{I} = \frac{1}{\omega_0 RC}$$

$$\therefore \frac{I_L}{I} = Q = \frac{1}{\omega_0 RC} \quad \text{----- (7)}$$

